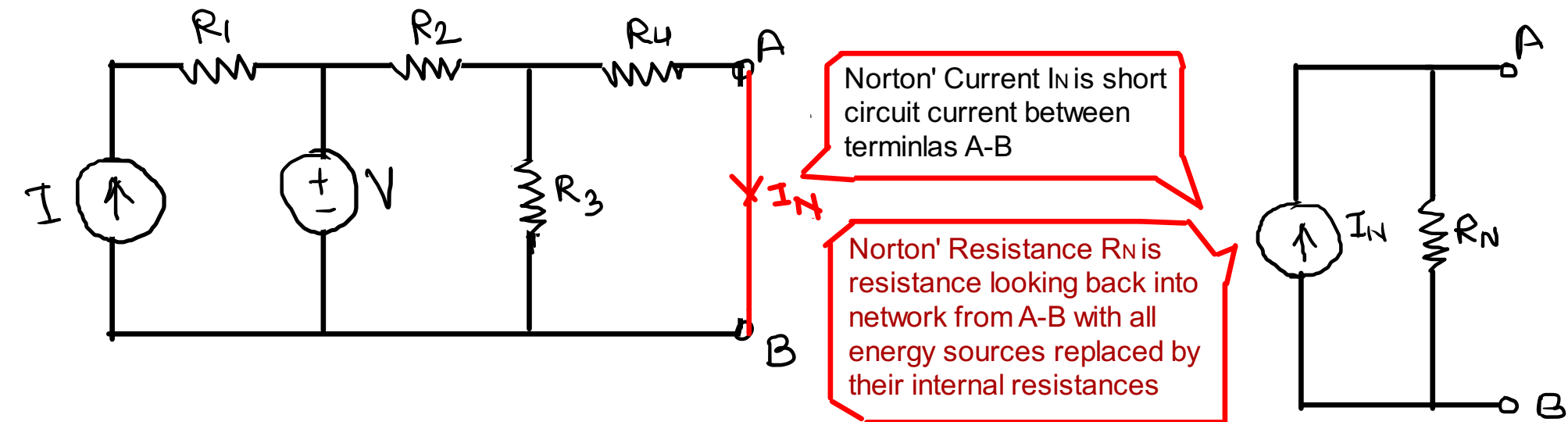


# Norton's Theorem


## Statement:

Any linear, active bilateral network can be replaced by a current source ( $I_N$ ) in parallel with a resistance ( $R_N$ ) where  $I_N$  is the short-circuit current (i.e. current through the two terminals when  $R_L$  is removed) and  $R_N$  is the internal resistance of the network as viewed back into the open-circuited network from terminals A and B with all energy sources replaced by their internal resistance (if any) and current sources by infinite resistance.




# Norton's Theorem

Given Network

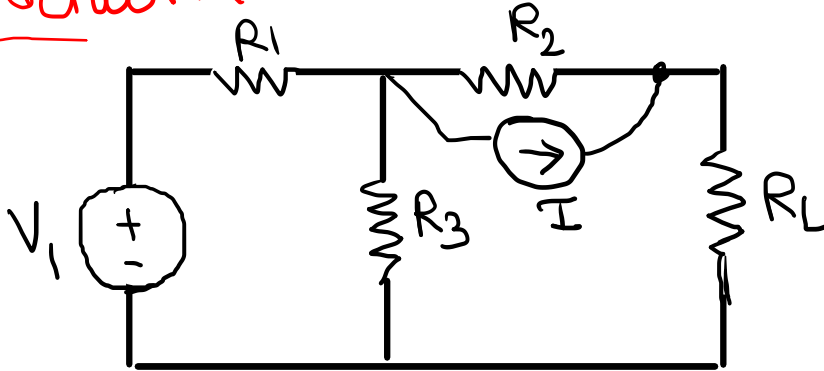


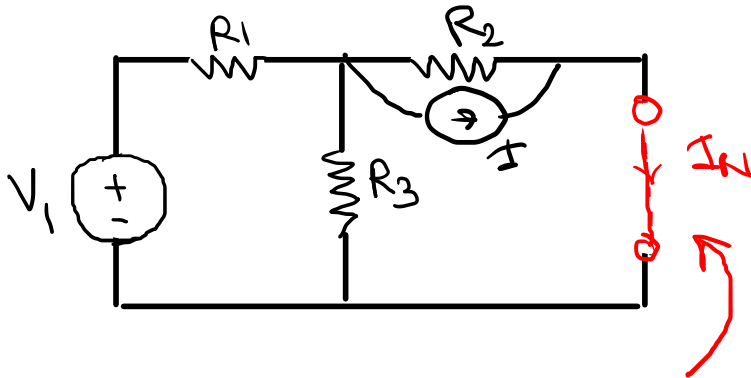1. Remove the load  $R_L$  from the circuit




2. Find  $I_N$  i.e. the short circuit current between the terminals (A-B) from where the load is removed, using any suitable method (mesh, nodal, source transformation etc..)

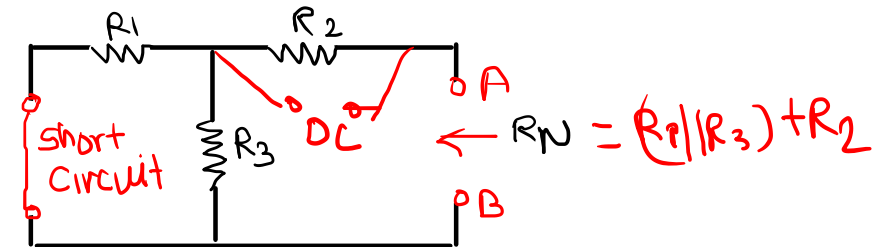
3. Find  $R_N$  i.e. resistance looking back into the network from the terminals (A-B) from where the load is removed with energy sources replaced by their internal resistances.



4. Draw Norton's equivalent circuit

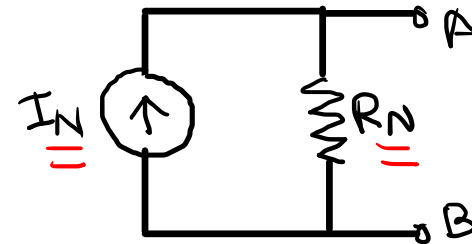


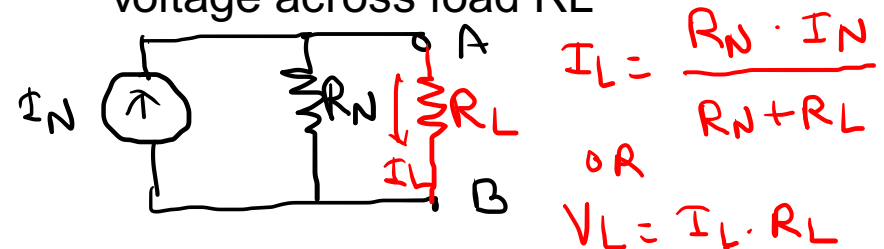5. Connect the load  $R_L$  and find current/voltage across load  $R_L$




# Relation between Thevenin and Norton Equivalent Circuit

Thevenin's Equivalent Circuit

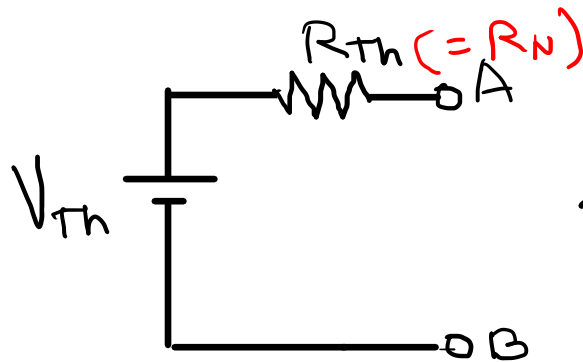

Norton's Equivalent Circuit

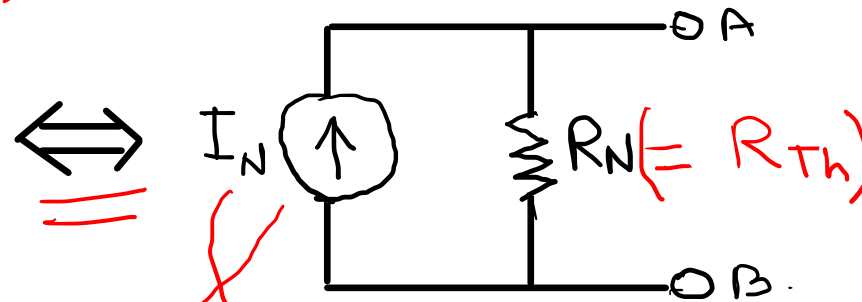

$$V_{Th} = I_N \cdot R_N$$

$$I_N = \frac{V_{Th}}{R_{Th}}$$

Norton's equivalent circuit can be obtained by applying source transformation to Thevenin's equivalent circuit.


Also

Thevenin's equivalent circuit can be obtained by applying source transformation to Norton's equivalent circuit.


# Norton's Theorem

Q.1 Find current flowing through 10 Ohm resistance using Norton's theorem


$$I_{10} = 0.46A$$

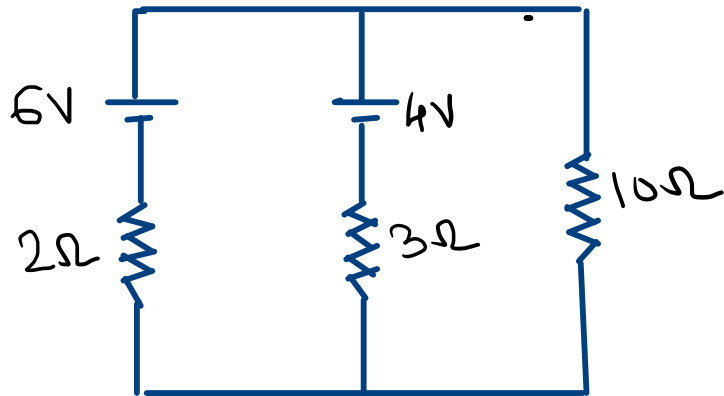

① Remove load  $R_L = 10\Omega$

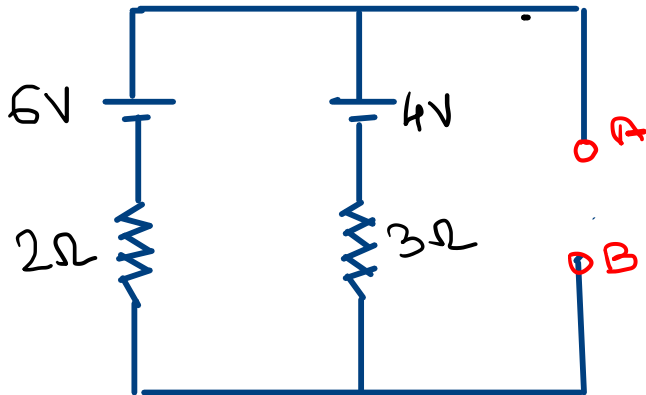

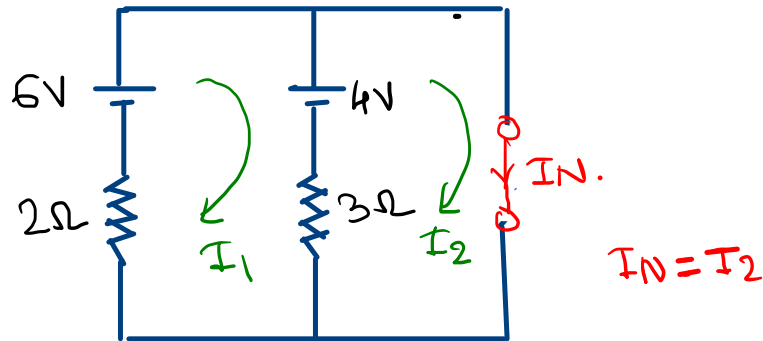② Short circuit A & B & find  $I_N = I_{sc}$



$$I_N = I_2$$

→ Using mesh Analysis.

$$\begin{aligned} \text{Mesh ①} \quad -2I_1 + 6 - 4 - 3(I_1 - I_2) &= 0 \\ 5I_1 - 3I_2 &= 2 \quad \text{--- ①} \end{aligned}$$


$$\begin{aligned} \text{→ mesh ②} \quad -3(I_2 - I_1) + 4 &= 0 \\ 3I_1 - 3I_2 &= -4 \quad \text{--- ②} \end{aligned}$$

$$\text{Solving ① \& ②} \quad I_1 = 3A \quad I_2 = 4.33A$$

# Norton's Theorem


Q.1 .....

③ Find  $R_N = R_{eq}$ .

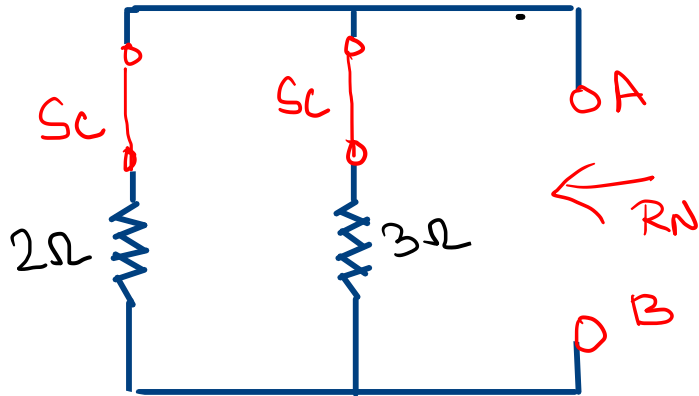

$$R_N = 2 \parallel 3 = \frac{6}{5} = 1.2 \Omega$$

④ Draw Norton's Equivalent Circuit

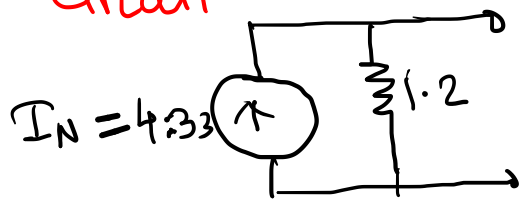


⇒

Source transformation (Thevenin's Equivalent)

$$V_{Th} = 4.33 \times 1.2 = 5.2$$

⑤ Connect  $R_L = 10 \Omega$

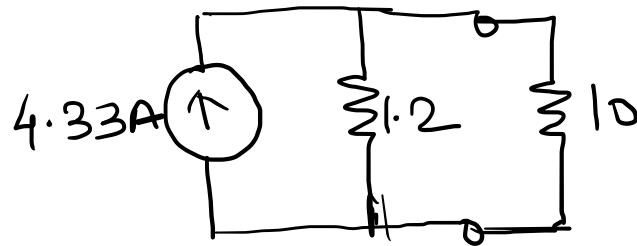


using current division formula

$$I_{10\Omega} = \frac{1.2 \times 4.33}{1.2 + 10}$$


$$\underline{I_{10\Omega} = 0.46 A}$$

$$I_{10} = 0.46 A$$




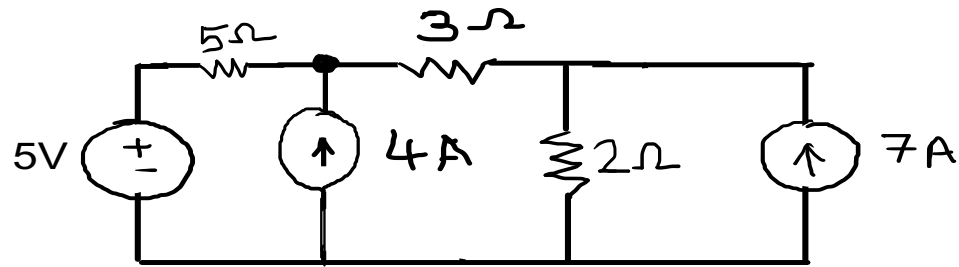
Example:- 2. Find voltage across 2 Ohm resistor using Norton's Theorem




① Remove  $R_L = 2\Omega$  & find  $I_N$

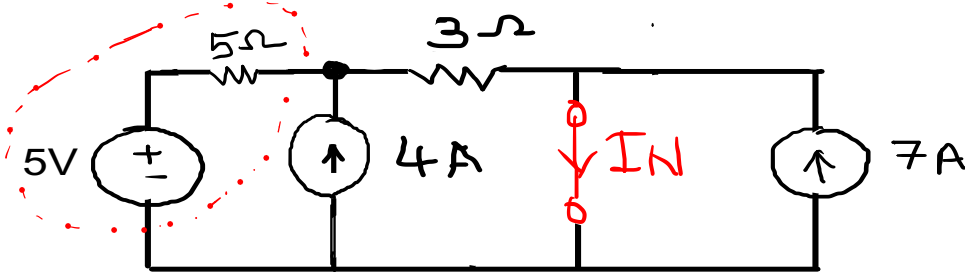

using source transformation

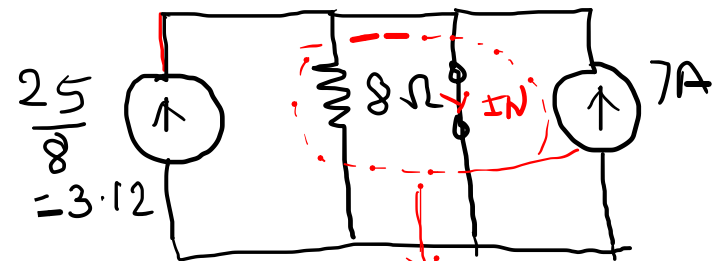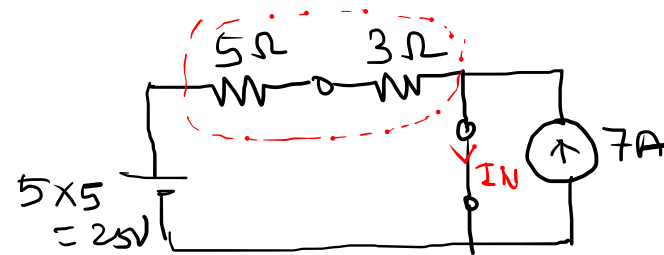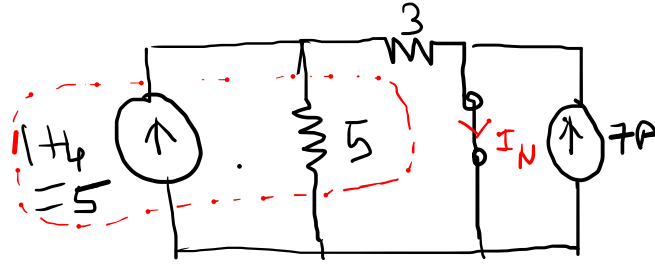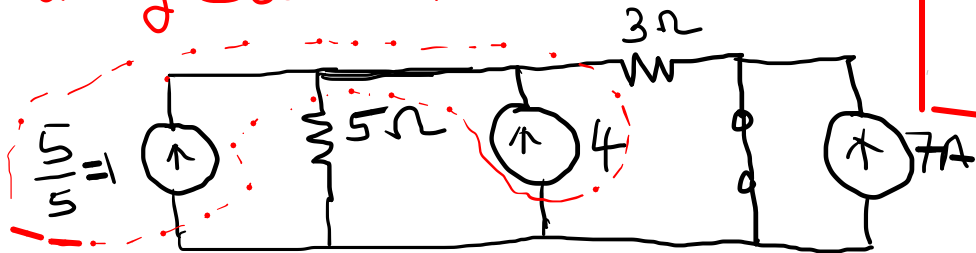

Short circuit (8Ω)

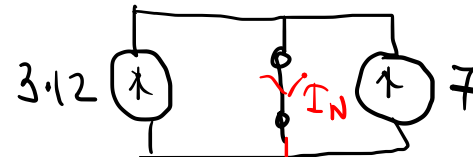

$$I_N = 3.12 + 7$$

$$I_N = 10.12 \text{ A}$$

$$I_N = \frac{81}{8}$$


$$R_N = 8\Omega$$

$$I_{2\Omega} = \frac{81}{10}$$

$$V_{2\Omega} = 16.2$$


Example:- 2. ....

③ Find  $R_N$

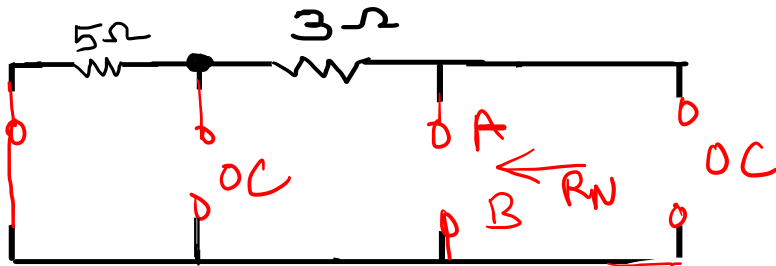

$$R_N = 5 + 3 = 8\Omega$$

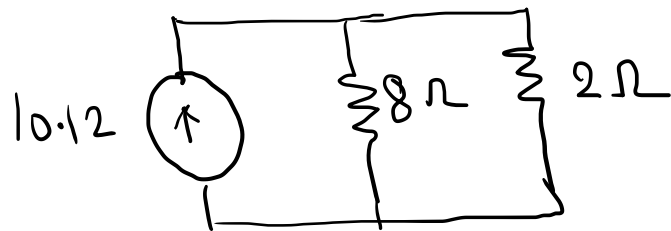④ Draw Norton's Equivalent circuit & Connect load.



Using Current division

$$I_{2\Omega} = \frac{10.12 \times 8}{10}$$

$$I_{2\Omega} = 8.09 \text{ A}$$

$$V_{2\Omega} = I_{2\Omega} \times 2$$

$$= 8.09 \times 2$$

$$\underline{V_{2\Omega} = 16.2 \text{ V}}$$

$$I_N = \frac{81}{8}$$

$$R_N = 8\Omega$$

$$I_{2\Omega} = \frac{81}{10}$$

$$V_{2\Omega} = 16.2$$

Example:- 3. Find current flowing through 1 Ohm resistor.

