

<b>Course Name:</b>	<b>Elements of Electrical and Electronics Engineering</b>	<b>Semester:</b>	<b>II</b>
<b>Date of Performance:</b>	<b>June '21</b>	<b>Batch No:</b>	<b>E1</b>
<b>Faculty Name:</b>		<b>Roll No:</b>	<b>16010321005</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	<b>/ 25</b>

## Experiment No: 10

### Title: Inverting and Non-inverting amplifier using OPAMP

#### Aim and Objective of the Experiment:


- To understand the open loop configuration of OPAMP
- To understand the concept of negative feedback and closed loop configuration of OPAMP.
- To understand inverting and Non-inverting amplifier of OPAMP
- To find gain of inverting and non-inverting amplifiers

#### COs to be achieved:


**CO5:** Understand operational amplifier and its applications

#### Circuit Diagram/ Block Diagram:


##### Pin diagram of IC 741

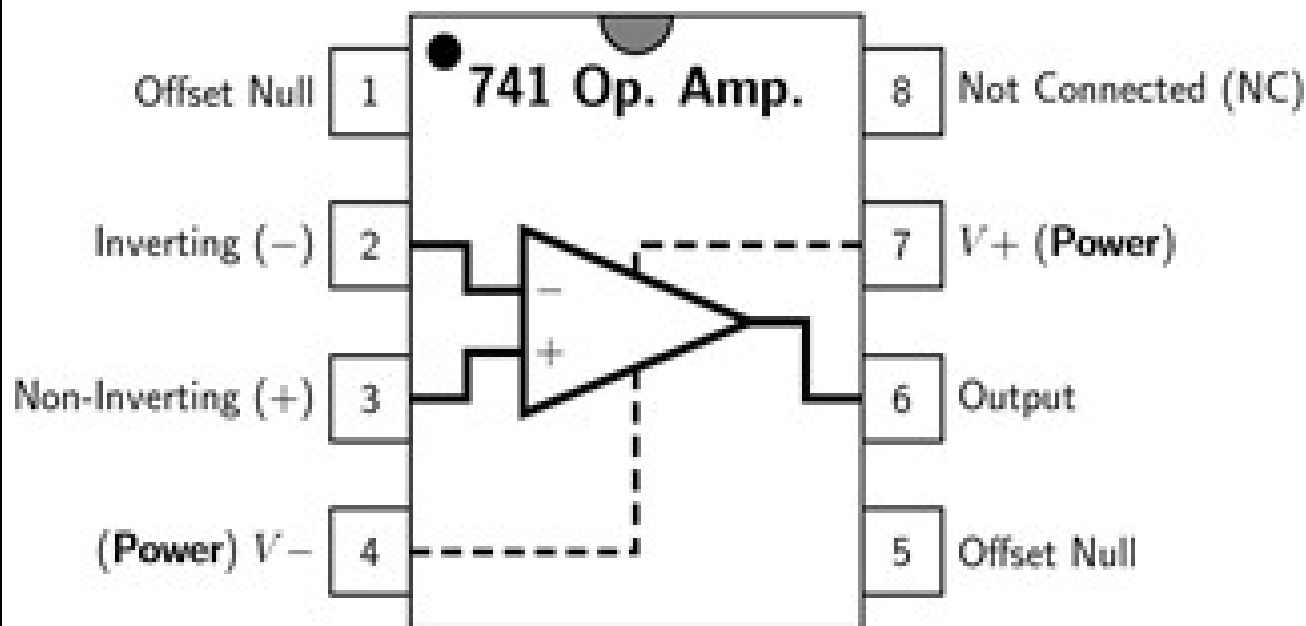

### 1. Inverting Amplifier

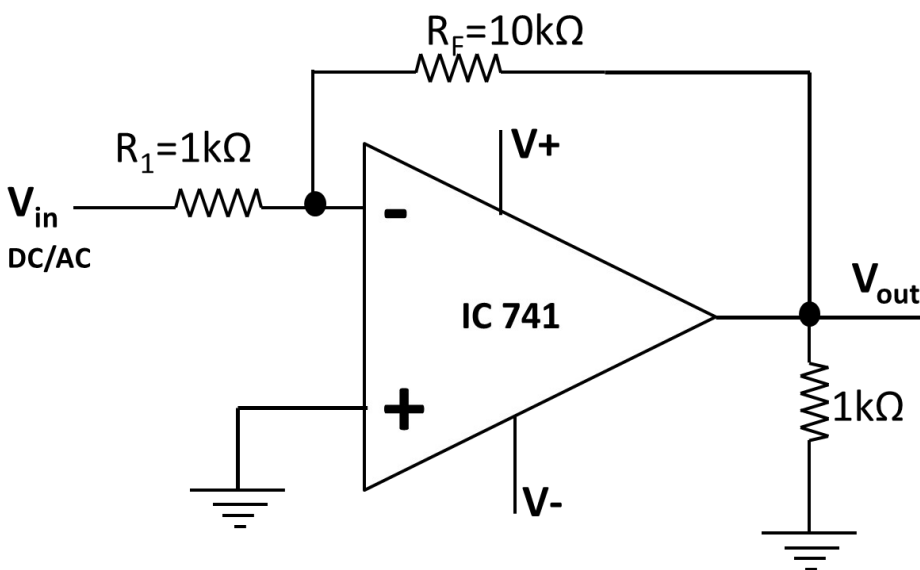

### 2. Non-inverting Amplifier

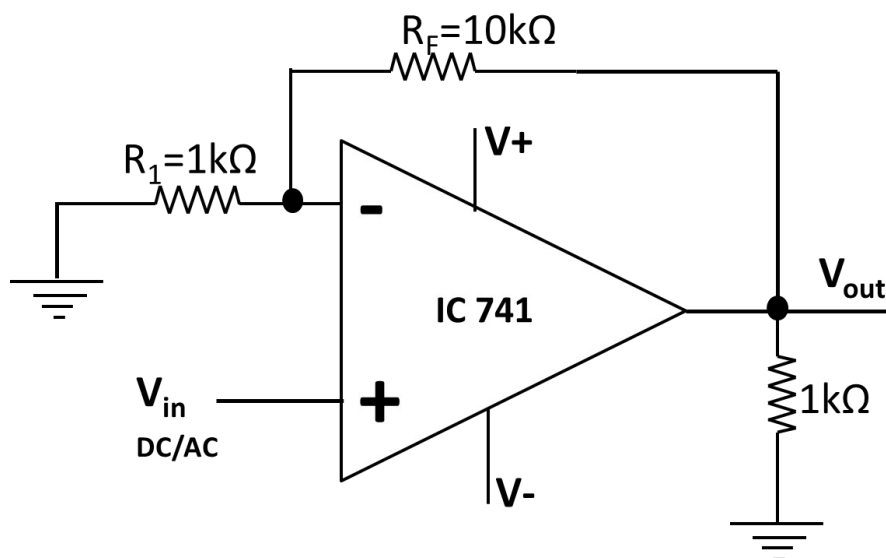

### Observation Table:

#### 1. A. Inverting Amplifier: DC input Voltage

Sr.No.	Vin (V)	Vout (V)	Practical Gain = Vout/Vin	Theoretical Gain = -RF/R1
1.	0.2	-0.99	-4.95	-5.00
2.	0.5	-2.49	-4.98	-5.00
3.	1.0	-4.99	-4.99	-5.00

### 1. B. Inverting Amplifier: AC input Voltage

Sr.No.	Frequency (Hz)	Vin(p-p) (V)	Vout(p-p) (V)	Practical Gain = Vout/Vin	Theoretical Gain = -RF/R1
1.	1 K	0.5	-2.50	-5.00	-5.00
2.	1 K	1.0	-5.00	-5.00	-5.00
3.	1 K	2.0	-10.00	-5.00	-5.00

### 2. A. Non-inverting Amplifier: DC input Voltage


Sr.No.	Vin (V)	Vout (V)	Practical Gain = Vout/Vin	Theoretical Gain = 1+RF/R1
1.	0.2	1.21	6.05	6.00
2.	0.5	3.01	6.02	6.00
3.	1.0	6.01	6.01	6.00

### 2. B. Non-inverting Amplifier: AC input Voltage


Sr.No.	Frequency (Hz)	Vin(p-p) (V)	Vout(p-p) (V)	Practical Gain = Vout/Vin	Theoretical Gain = 1+RF/R1
1.	1k	0.5	3.00	6.00	6.00
2.	1k	1.0	6.00	6.00	6.00
3.	1k	2.0	12.00	6.00	6.00

Outputs:


Inverting DC:

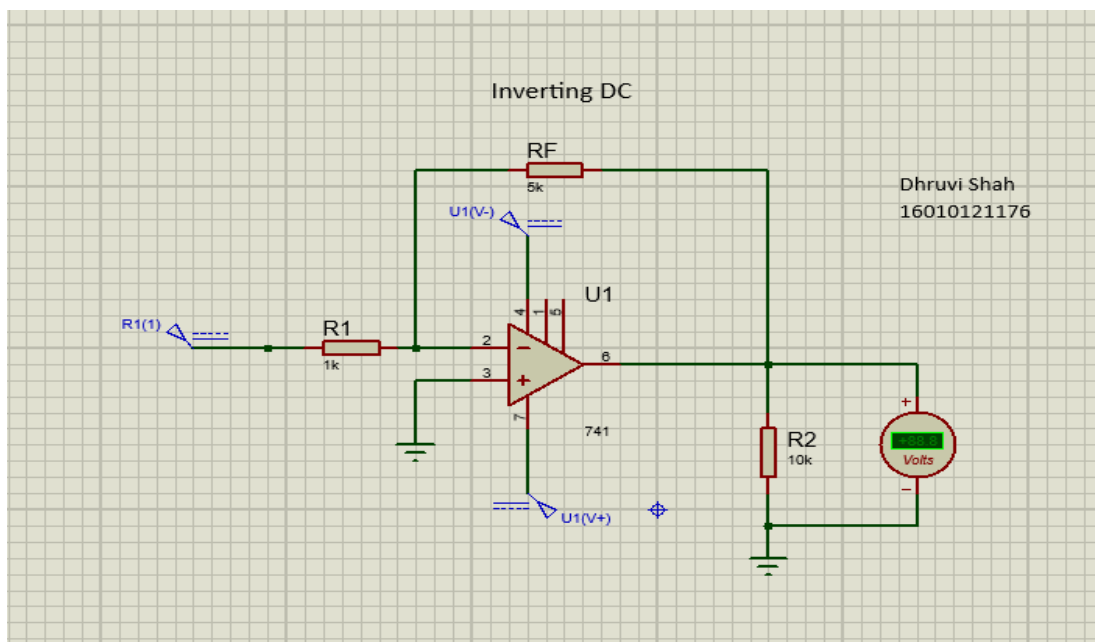


## Inverting AC:

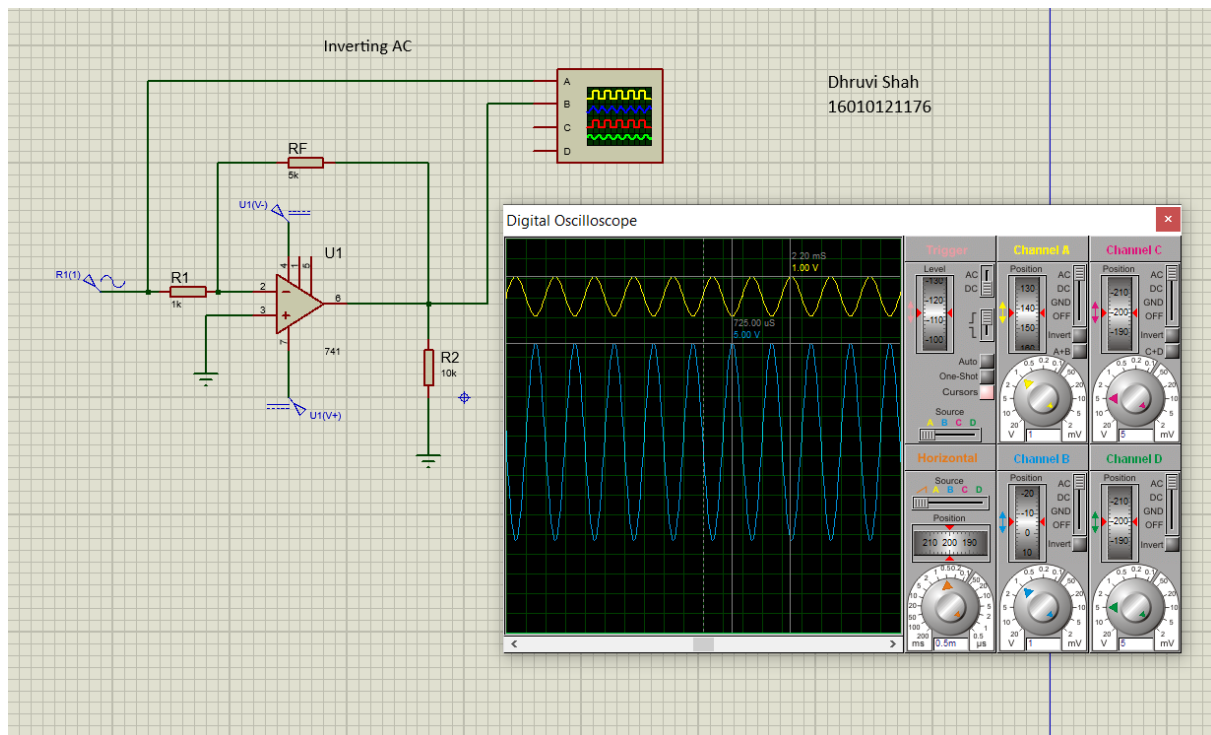

## Non-Inverting DC:

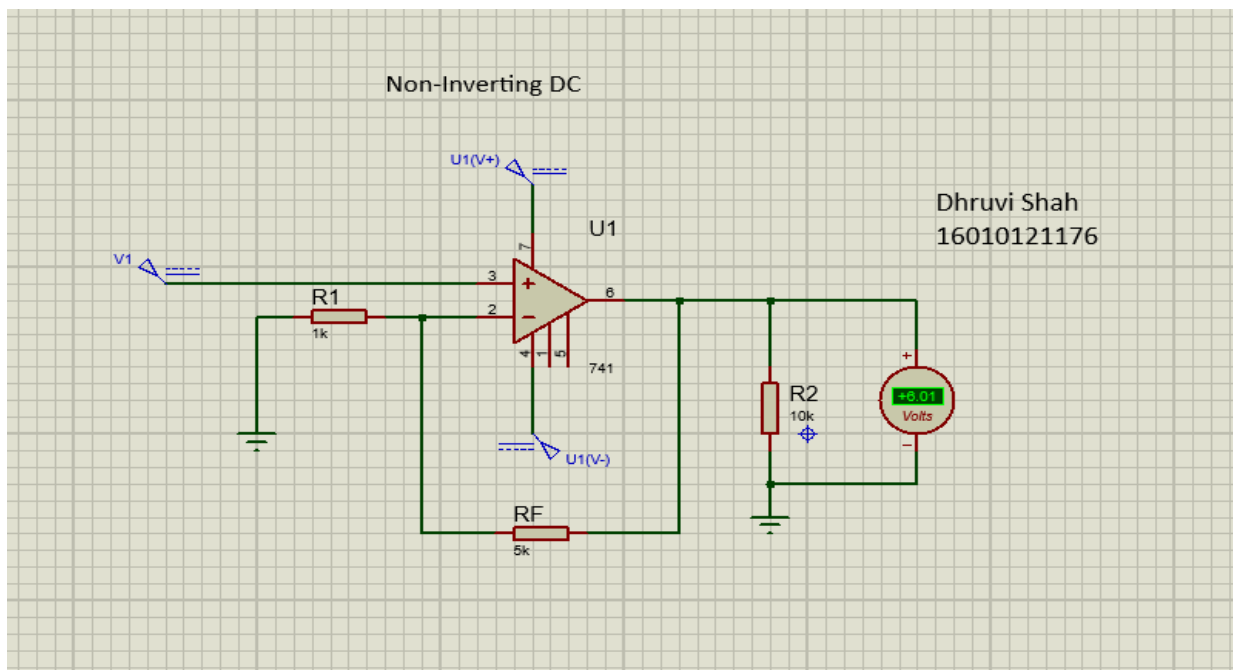

## Non-Inverting AC:

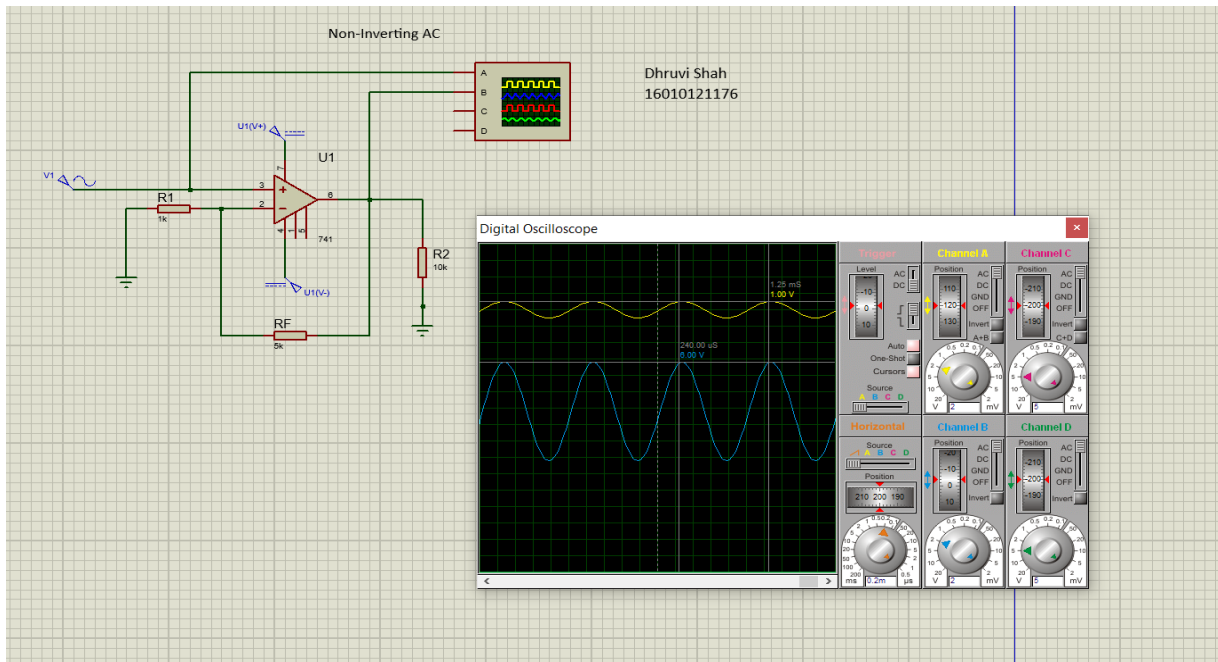

## Post Lab Subjective/Objective type Questions:

1. List the characteristics of Ideal operational amplifier.

Characteristics of an Ideal Operational Amplifier are:

Infinite open-loop gain  $G = V_{out} / V_{in}$

Infinite input impedance  $R_{in}$ , and so zero input current

Zero input offset voltage

Infinite output voltage range

Infinite bandwidth with zero phase shift and infinite slew rate

Zero output impedance  $R_{out}$ , and so infinite output current range

Zero noise

2. List the important parameters of IC 741 operational amplifier.

Important parameters of IC 741 Op-amp are:

- (1) Open loop gain
- (2) Input impedance
- (3) Output impedance
- (4) CMRR
- (5) Input Offset voltage and current
- (6) Output offset voltage and current
- (7) Gain Bandwidth product
- (8) Power supply voltage

**Conclusion:**

We have understood the open loop configuration of OPAMP and closed loop configuration of OPAMP, inverting and non-inverting amplification of OPAMP and to find the gain of inverting and non-inverting amplifiers.

**Signature of faculty in-charge with Date:**