

<b>Course Name:</b>	<b>EEEE</b>	<b>Semester:</b>	<b>II</b>
<b>Date of Performance:</b>	<b>06/01/2022</b>	<b>Batch No:</b>	<b>E1</b>
<b>Faculty Name:</b>	<b>June '22</b>	<b>Roll No:</b>	<b>16010321005</b>
<b>Faculty Sign &amp; Date:</b>		<b>Grade/Marks:</b>	

**Experiment No: 8**  
**Title: Power factor improvement (parallel)**

**Aim and Objective of the Experiment:**


- To improve power factor of a single phase inductive AC circuit using capacitor across the load.

**Requirements:**


Inductor box, 1 K $\Omega$ -3W Resistor, Capacitor box, AC Ammeter and AC Voltmeter.

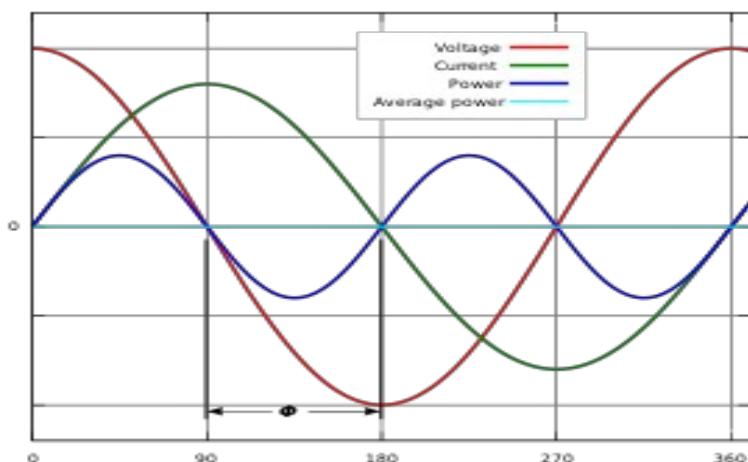**Theory:**


When we need to convert electrical energy to mechanical energy, electric motors are used for it. These AC motors convert electric energy in two forms namely mechanical energy in the form of rotary motion and other is magnetic field. Magnetizing currents are lagging to the supply voltage. This magnetic energy is not a mechanical energy so it is kind of wastage, but without which motor will not run and convert electric energy into mechanical energy. Such form of energy is called as reactive power. Reactive power must be as less as possible so that the load will utilize maximum power and current requirement will be less for the same amount power. As the current requirement is less, so wire thickness will be small in diameter. Installation cost and energy cost will be also reduced. To reduce reactive power of the circuit, different power factor improvement methods are used. One of the most familiar method is the use of capacitor bank. We can use capacitor in series with the load or across the load. Following diagrams are illustrating effect of PF on active power.



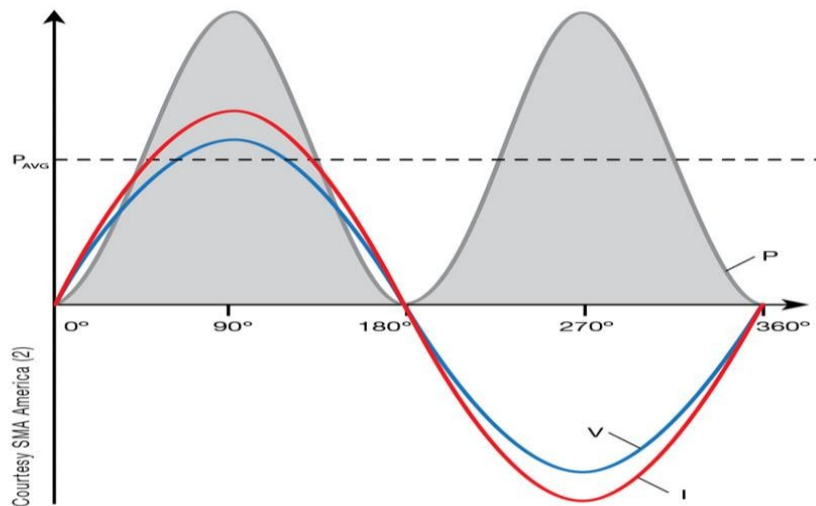
In the above figure instantaneous and average power calculated from AC voltage and current with a zero power factor. The blue line shows all the power is stored temporarily in the load during the first quarter cycle and returned to the grid during the second quarter cycle, so no real power is consumed by the load which is shown by sky-blue colour line.



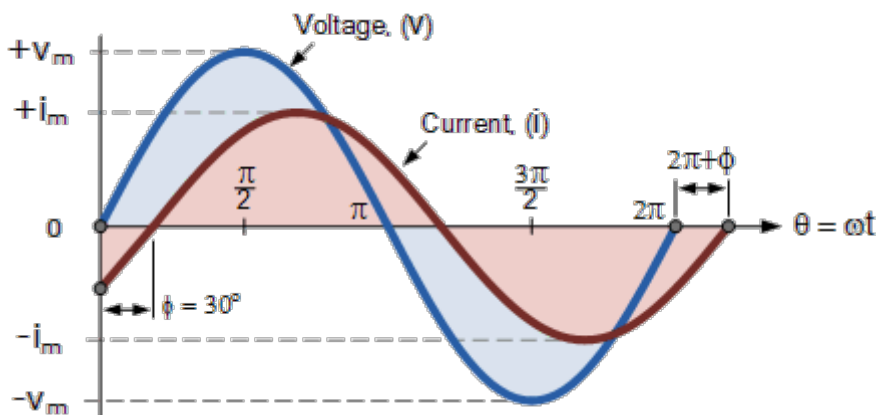In the above figure instantaneous and average power calculated from AC voltage and current with a unity power factor. The gray part shows all the power is absorbed in the load during the first half cycle as well as the second half cycle, so real power is fully consumed.



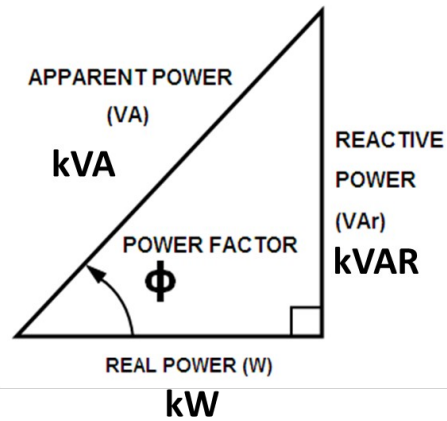When power factor is between zero and unity, then real power consumed by the load depends upon PF of the circuit. Greater the power factor is always better to consume power.




$$\text{Power Factor} = \frac{\text{True Power}}{\text{Apparent Power}}$$


$$\text{Power Factor} = \cos \phi = \frac{\text{kW}}{\text{kVA}}$$

### Circuit Diagram/ Block Diagram:

RL Circuit in series

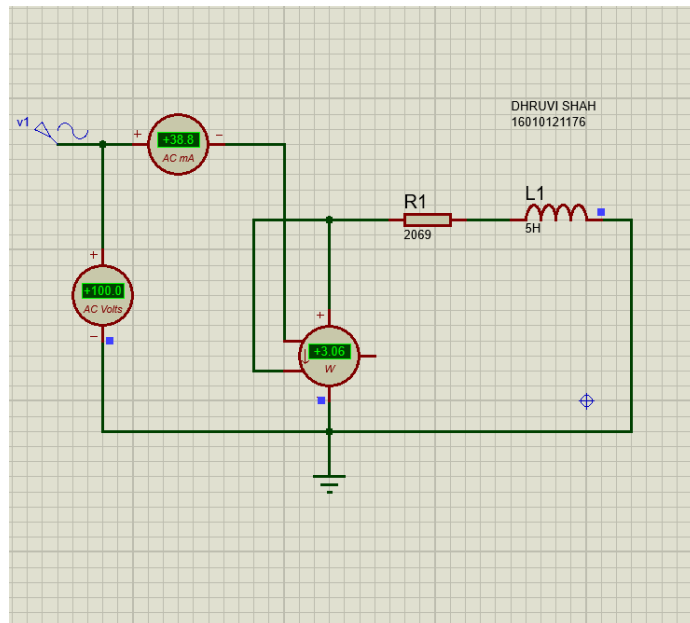

### RLC Circuit in parallel

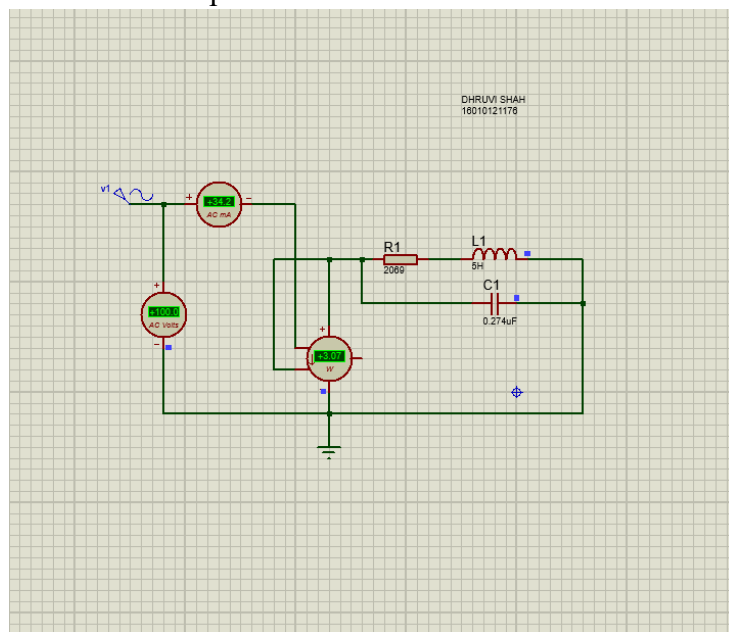

#### Stepwise-Procedure:

1. Connect series R and L circuit across 230V, 1 $\phi$ , 50 Hz AC supply and note down circuit voltage and current.
2. Calculate practical value of circuit power factor by taking ratio of active power (P) and apparent power (S).
3. Connect required value of capacitor in parallel with R-L load and switch on power supply to note circuit voltage and current.
4. Calculate practical value of circuit power factor by taking ratio of active power (P) and apparent power (S).
5. Compare theoretical and practical values of PF before connecting the capacitor and after connecting capacitor.

#### Observation Table:

Sr No	Type of load	Voltage (V)		Current (I) (mA)		P (W)= (I <sub>coil</sub> ) <sup>2</sup> x R		S (VA) V <sub>X</sub> I <sub>n</sub>		Power factor	
		Th	Pr	Th	Pr	Th	Pr	Th	Pr	Th	Pr
1	R-L	100	100	38.5	38.8	3.066	3.06	3.85	3.88	0.7966	0.7912
2	R-L-C	100	100	34.065	34.2	3.065	3.07	3.42	3.42	0.9	0.897

### 1. Calculations of R-L circuit.

Calculations for RL Circuit  

$$X_L = 2\pi fL$$

$$= 2 \times 3.14 \times 50 \times 5$$

$$= 1570 \Omega$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{(2069)^2 + (1570)^2} = 2597.2$$

$$\tan^{-1} \phi = \frac{X_L}{R} = \frac{1570}{2069} = 0.758$$

$$\phi = \tan^{-1} (0.758)$$

$$= 37.19^\circ$$

$$P.F = \cos \phi = \cos 37.19 = 0.7966$$

$$I = \frac{V}{Z} = \frac{100}{2597.2} = 0.0385 A$$

$$= 38.5 mA$$

$$S = VI = 100 \times 38.5 = 3850 VmA$$

$$= 3.85 VA$$

$$P = I^2 R = (38.5)^2 (2069) = 3066.775 mW$$

$$= 3.066 W$$

$$P.F = \frac{P}{S} = \frac{3.066}{3.85} = 0.7946$$

## 2. Finding C for Pf=0.9

Finding C for  $P_f = 0.9$

$$P_f = \cos \phi_n = 0.9$$

$$\phi_n = \cos^{-1}(0.9)$$

$$= 25.84$$

$$I_R = I \sin \phi = 32.5 \times \sin(37.19) = 38.5 \times 0.6$$

$$= 23.27 \text{ mA}$$

$$I_n = \frac{P_n}{V \cos \phi_n} = \frac{3.066}{100 \times 0.9} = 0.034065 \text{ A}$$

$$I_n = 34.065 \text{ mA}$$

$$I_{Rn} = I_n \sin \phi_n = 34.065 \times \sin(25.84)$$

$$= 14.84 \text{ mA}$$

$$I_c = I_R - I_{Rn} = 23.27 - 14.84$$

$$= 8.5 \text{ mA}$$

$$X_C = \frac{V}{I_c} = \frac{100}{8.5} = 11.7642 \text{ m}\Omega$$

$$= 11764.7 \Omega$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2 \times 3.14 \times 50 \times 11764.7}$$

$$= 27.07 \times 10^{-7}$$

$$= 0.2707 \mu\text{F}$$

$$S = VI = 100 \times 34.065 = 3406.5 \text{ VmA}$$

$$= 34065 \text{ VA}$$

$$P_{AV} = P = 3.066 \text{ W}$$

## 3. Calculations for R-L and C in parallel to verify PF

$$P.F = \frac{P_N}{S} = \frac{3.066}{3.4065} = 0.9$$



**Post Lab Subjective/Objective type Questions:**

**1. What are benefits of connecting capacitor across the load to improve circuit PF?**

Improving the PF can maximize current-carrying capacity, improve voltage to equipment, reduce power losses, and lower electric bills. The simplest way to improve power factor is to add PF correction capacitors to the electrical system. PF correction capacitors act as reactive current generators.

To improve power factor, the capacitor should be connected in parallel, because in parallel connection the capacitance of the capacitor increases. So, when the capacitance of the capacitor increases it delivers more reactive power to the load so the power factor shall be improved.

**Conclusion:**

We learnt how to improve power factor of a single phase inductive AC circuit using capacitor across the load

**Signature of faculty in-charge with Date:**