

Q1. A.

1. Transformer (b)
2. Emitter and collector both junctions are reversed biased (b)
3. Fleming's Left hand rule (d)
4. 55.2 W (a)
5. Lags behind the voltage by  $90^\circ$  (a)
6.  $90^\circ$  (c)
7. Commutator (c)
8. f (a)
9. Infinite (c)
10. 10 (a)

Q1. B

1. Neat and labelled Diagram 1 mks.

i/p and o/p waveform

Gain Equation

}

1 mks

2. EMF equation of Transformer

The sinusoidal voltage is applied to primary winding. This produces the flux  $\phi$ , given by

$$\phi = \phi_m \sin \omega t$$

According to Faraday's Law of Electromagnetic Induction, self induced emf is given by,

$$e_1 = -N_1 \frac{d\phi}{dt}$$

$$e_1 = -N_1 \frac{d(\phi_m \sin \omega t)}{dt}$$

$$\Rightarrow e_1 = -N_1 \omega \cos \omega t \phi_m$$

$$e_1 = +N_1 \phi_m \omega \sin(\omega t - 90^\circ) \quad \text{--- 1mk}$$

$\Rightarrow$  Self induced emf lags behind flux by  $90^\circ$

$$\therefore e = E_m \sin(\omega t \pm \phi)$$

$$E_m = N_1 \phi_m \omega$$

rms value of induced emf  $\Rightarrow E_1 = \frac{E_m}{\sqrt{2}} = \frac{N_1 \phi_m \omega}{\sqrt{2}} = \frac{N_1 \phi_m 2\pi f}{\sqrt{2}}$

$$E_1 = 4.44 f N_1 \phi_m \quad V$$

My rms value of induced emf in secondary winding  $E_2 = 4.44 f N_2 \phi_m \quad V$  } 1mk

③  $V = 141.4 \sin 314t$

$\omega = 314$

frequency  $= \frac{314}{2\pi} = 50 \text{ Hz}$

$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 99.98 \text{ V}$

$V_{avg} = 0.637 V_m = 0.637 \times 141.4 = 90.018 \text{ V}$

At  $t = 3 \text{ msec} \Rightarrow v = 141.4 \sin \left( 314 \times 3 \times 10^{-3} \times \frac{180}{\pi} \right)$  } 1mk

$v = 114.35 \text{ V}$

Soln

④ Output Characteristics of npn transistor  
In CE mode


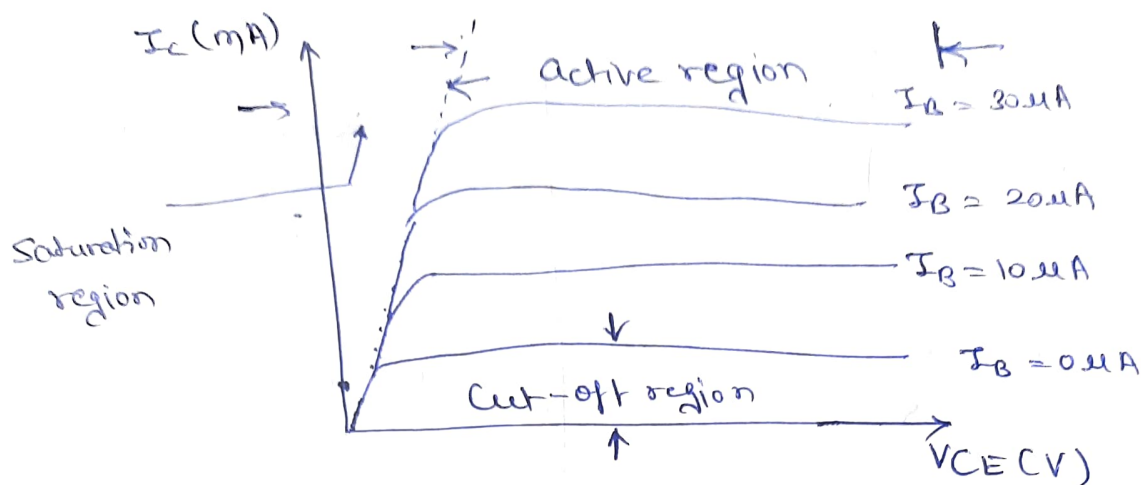


Diagram — 1mk

Explanation — 1mk

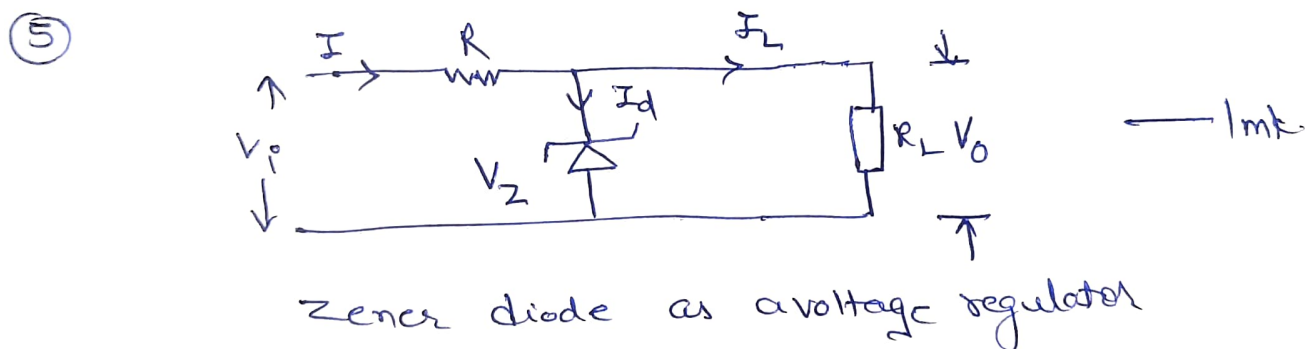

→ Explanation


—— 1mk

⑥ Any four advantages of  
three phase over single phase AC — 2mk

⑦

⑦ Impedance Triangle of a series RLC circuit


if  $X_L > X_C$  &  $Z = R + jX$

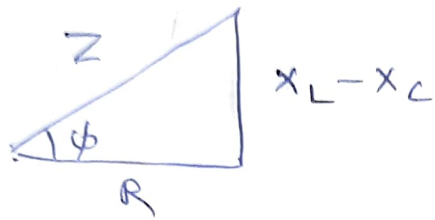

$$\cos \phi = \frac{R}{Z}$$

$$\bar{Z} = Z \angle \phi$$


if  $X_L < X_C$  &  $Z = R - jX$

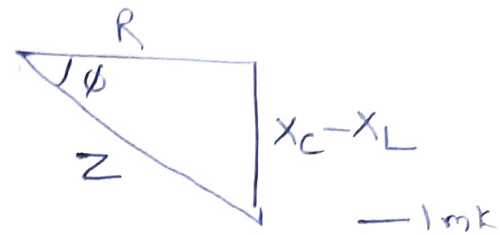

$$\cos \phi = \frac{R}{Z}$$

$$\bar{Z} = Z \angle -\phi \quad \left. \vphantom{\bar{Z}} \right\} \text{Im}$$

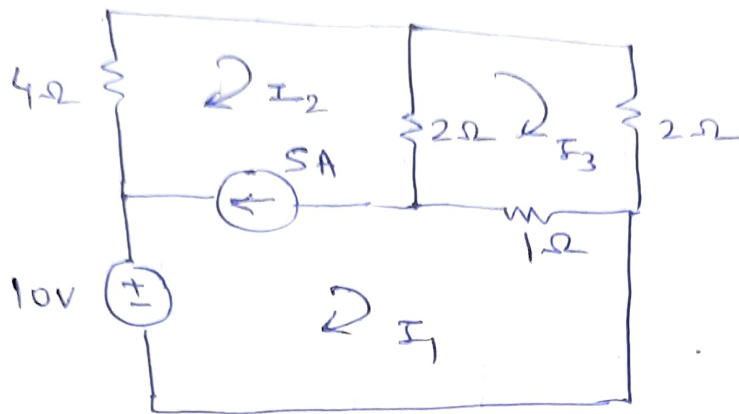Q.2 Find  $I_1$ ,  $I_2$  and  $I_3$  in given electrical n/w.



$$I_2 - I_1 = 5 \quad \text{--- (1)} \quad \text{--- 0.2 mk}$$

Writing supermesh eq<sup>n</sup>;

$$10 - 4I_2 - 2(I_2 - I_3) - 1(I_1 - I_3) = 0$$

$$-I_1 - 6I_2 + 3I_3 = -10 \quad \text{--- (2)} \quad \text{--- 0.2 mk}$$

KVL in loop (3)

$$-2(I_3 - I_2) - 2I_3 - 1(I_3 - I_1) = 0$$

$$I_1 + 2I_2 - 5I_3 = 0 \quad \text{--- (3)} \quad \text{--- 0.2 mk}$$

$$\begin{bmatrix} -1 & 1 & 0 \\ -1 & -6 & 3 \\ 1 & 2 & -5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ -10 \\ 0 \end{bmatrix} \quad \text{--- 0.1 mk}$$

$$\Rightarrow I_1 = -2.69 \text{ A} = -\frac{35}{13} \text{ A}$$

$$I_2 = 2.307 \text{ A} = \frac{30}{13} \text{ A}$$


$$I_3 = 0.384 \text{ A} = \frac{5}{13} \text{ A}$$

--- 0.3 mk


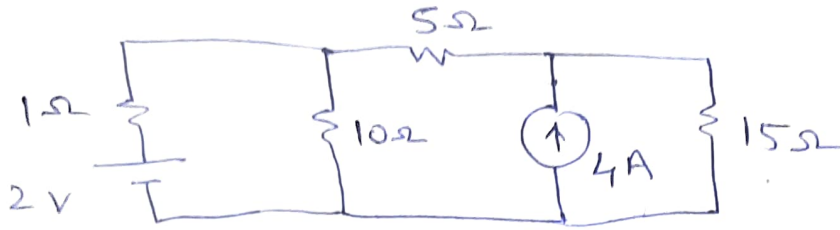
Q2a

OR



Calculate power dissipated in  $10\Omega$  using Norton's Theorem.



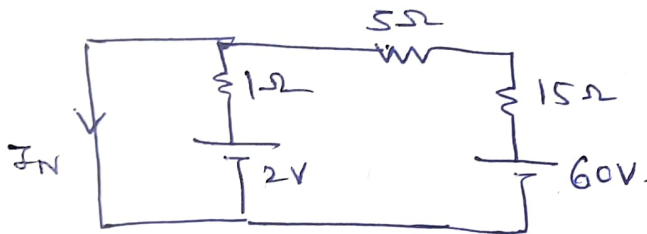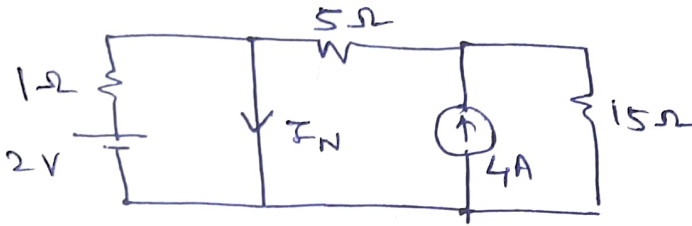
Step ① find Norton's Current; short circuit  $10\Omega$ .



using source transformation

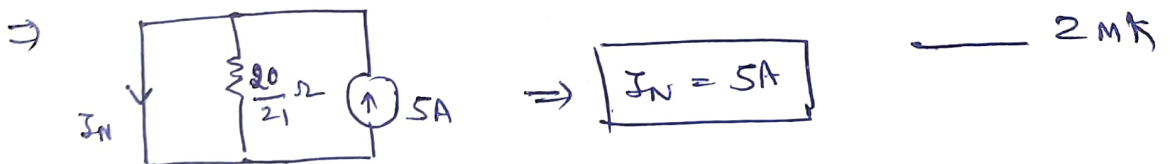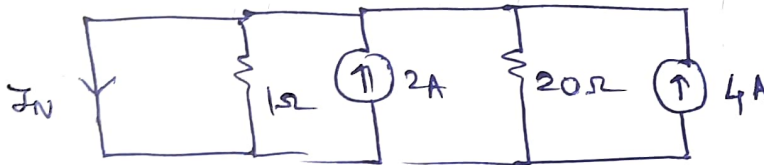


Step ② find  $R_N$

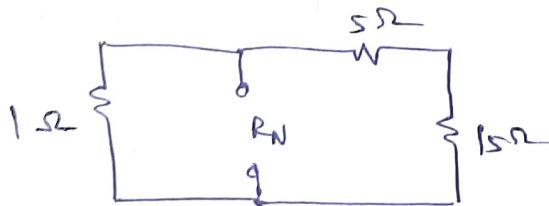

$$R_N = \frac{20 \times 1}{21} = \frac{20}{21} = 0.952\Omega$$

— 1mk

Step ③ Power in  $10\Omega$  resistance

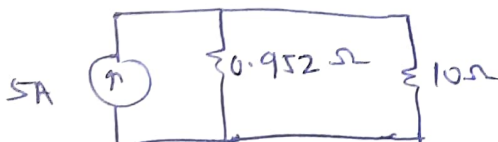


$$I_{10\Omega} = \frac{5 \times 0.952}{5 + 10} = 0.434A$$

$$P_{10\Omega} = I_{10\Omega}^2 R_{10\Omega} = (0.434)^2 \times 10$$


$$P_{10\Omega} = 1.88W$$

— 2mk

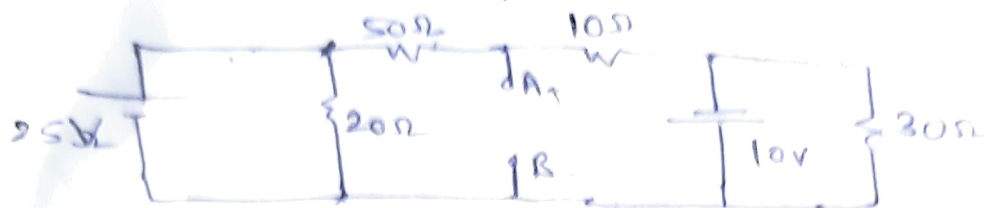26) find Thevenin's Equivalent across AB.



Step ① find  $V_{th}$

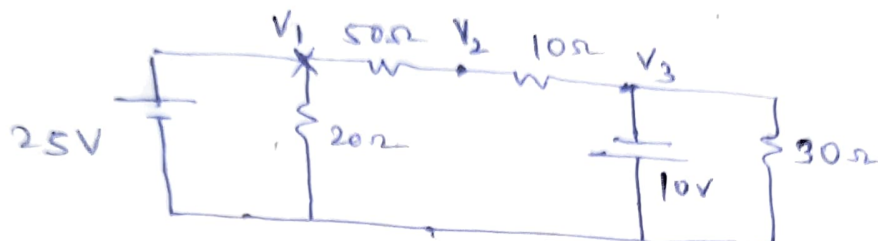

Apply KCL at  $V_1$  from ckt

$$V_1 = 25V \text{ and } V_3 = -10V \quad \text{--- ①}$$

Apply KCL at  $V_2$


$$\frac{V_2 - V_1}{50} + \frac{V_2 - V_3}{10} = 0$$

$$-\frac{1}{50}V_1 + \left(\frac{1}{50} + \frac{1}{10}\right)V_2 - \frac{1}{10}V_3 = 0 \quad \text{using ①}$$

$$\Rightarrow V_2 = V_{th} = -4.16V$$


--- 02m

Step ②

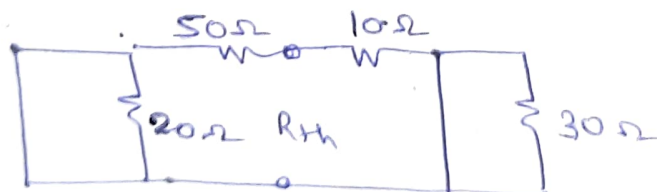

$$R_{th} = 50 || 10 = \frac{50 \times 10}{60} = 8.33\Omega \quad \text{--- 02m}$$

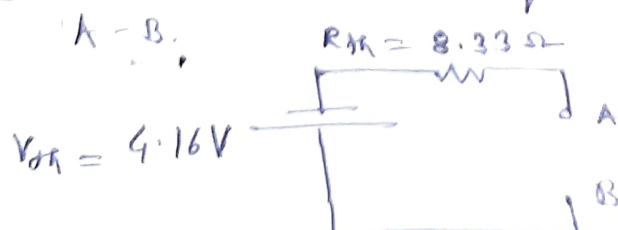Step ③ Thevenin's eqt ckt across terminal




--- 01m



Q.3a.

find  $C$  for unity power factor.

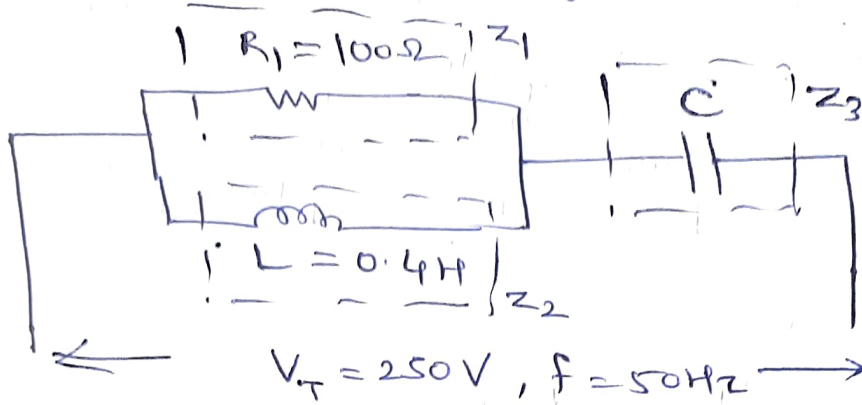

Soln

$$L = 0.4H$$

$$X_L = j2\pi fL = j125.66\Omega = j40\pi\Omega$$

$$\bar{Z}_1 = 100\Omega$$

$$\bar{Z}_2 = 40\pi\Omega$$

$$\bar{Z}_3 = -jX_C$$

$$\bar{Z}_T = (\bar{Z}_1 \parallel \bar{Z}_2) + \bar{Z}_3$$

$$\bar{Z}_T = \frac{(100)(j125.66)}{100 + j125.66} + (-jX_C)$$

$$= 61.22 + j48.72 - jX_C$$

$$\bar{Z}_T = 61.22 + j(48.72 - X_C)$$

$$\bar{Z}_T = Z_T \angle \phi_T$$

$$Z_T = \sqrt{(61.22)^2 + (48.72 - X_C)^2}$$

$$\phi_T = \tan^{-1} \left( \frac{48.72 - X_C}{61.22} \right)$$

Now, for unity power factor i.e.  $\cos \phi_T = 1$   
 $\phi_T = 0^\circ$

$$\Rightarrow 0 = \tan^{-1} \left( \frac{48.72 - X_C}{61.22} \right)$$

$$\Rightarrow \tan 0 = \frac{48.72 - X_C}{61.22}$$

$$\Rightarrow X_C = 48.72\Omega$$



$$\text{Now, } X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi \times 50 \times 48.72}$$

$$C = 6.53 \times 10^{-5} \text{ F}$$

OR

Q.3 (a)

A series RLC ckt

$$R = 10 \Omega, L = 0.01 \text{ H}, C = 100 \mu\text{F}$$

① Resonant frequency  $\omega_r = \frac{1}{\sqrt{LC}} = 845.15 \text{ rad/sec}$

1mk

② Q factor  $= \frac{1}{R} \sqrt{\frac{L}{C}} = 1.183$

1mk

③ Bandwidth (BW)  $= \frac{R}{L} = 714.28 \text{ rad/sec}$

1mk

④ Lower and upper frequency points of BW

$$\omega_H = \omega_r + \frac{BW}{2} = 1202.9 \text{ rad/sec}$$

$$\omega_L = \omega_r - \frac{BW}{2} = 488.01 \text{ rad/sec}$$

1mk

⑤ if  $V(t) = 1 \sin(1000t)$


$$\Rightarrow V_T = \frac{1}{\sqrt{2}} = 0.707 \text{ V}$$

$$V_C = \frac{V_T}{R} \sqrt{\frac{L}{C}}$$

$$= 0.836 \text{ V}$$

1mk

Q. 2 (b)

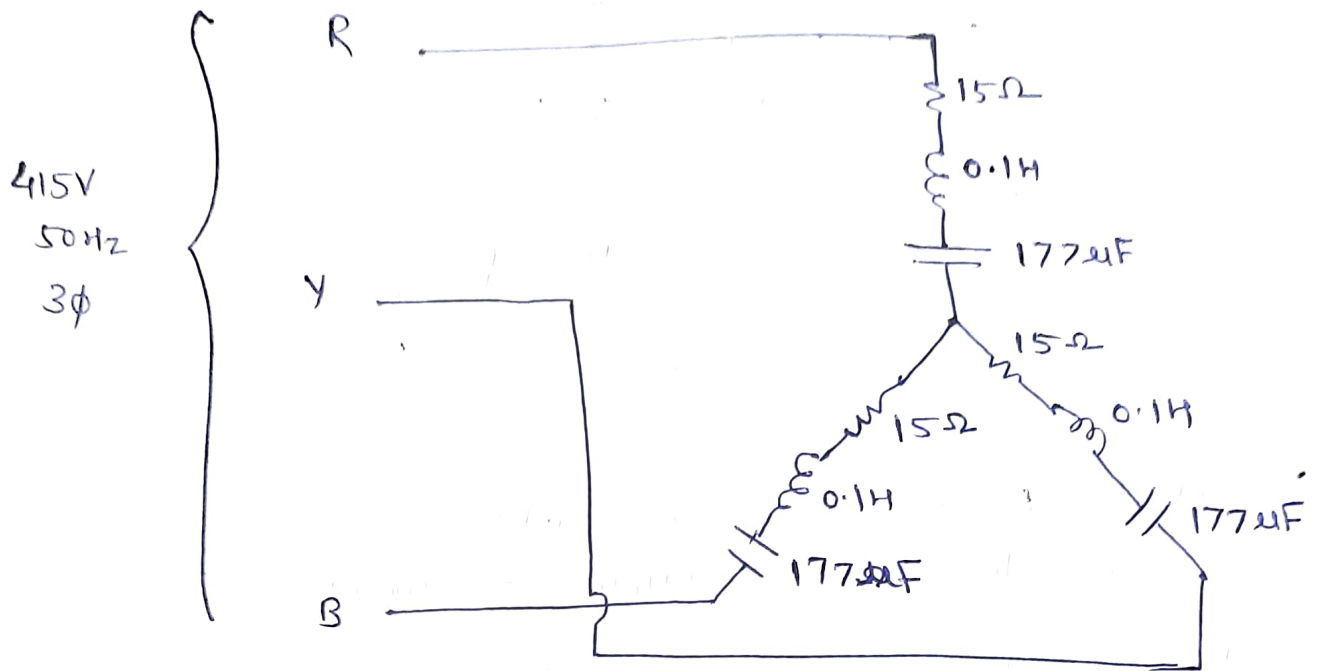

Soln —

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.1 = 31.41\Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 177 \times 10^{-6}} = 17.97\Omega$$

Impedance of each phase,

$$\bar{Z}_{ph} = R + jX_L - jX_C = 15 + j31.41 - j17.98$$

$$\bar{Z}_{ph} = 15 + j13.43 = 20.13 \angle 41.83^\circ \text{ — Impk}$$

for star connected

$$I_L = I_{ph} \quad \text{and} \quad V_L = \sqrt{3} V_{ph}$$

$$V_L = 415V \Rightarrow V_{ph} = 239.6V$$

$$I_L = I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{239.6}{20.13} = 11.9A \text{ — Impk}$$

$$pf = \cos \phi_{ph} = 0.745 \text{ (lag)} \text{ — Impk}$$


Active Power  $P_{3\phi} = \sqrt{3} V_L I_L \cos \phi_{ph}$

$$P_{3\phi} = 6373.61W \text{ — Impk}$$


Reactive Power  $Q_{3\phi} = \sqrt{3} V_L I_L \sin \phi_{ph}$

$$= 5704.67VAR \text{ — Impk}$$

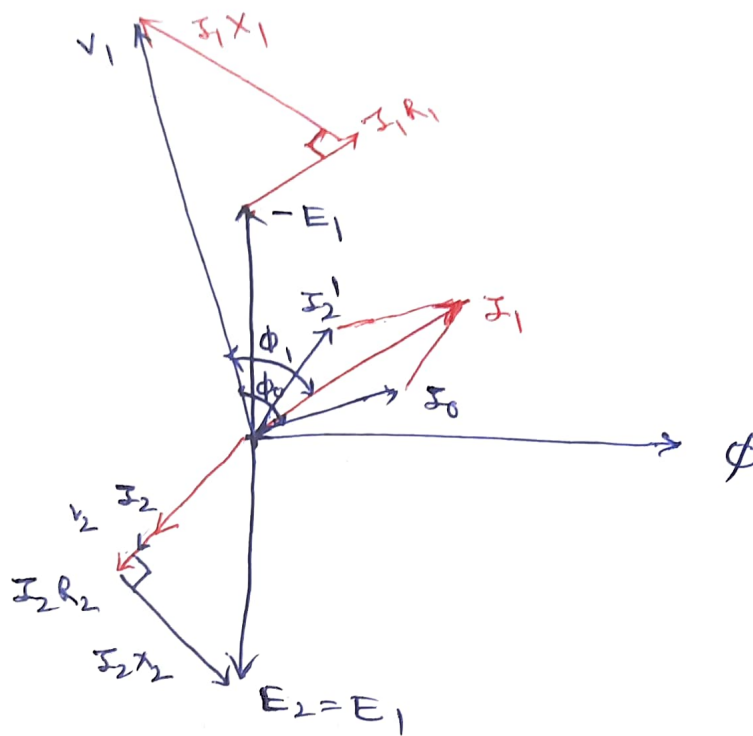Q.4a Phasor diagram considering winding resistance and magnetic leakage when load is resistive.



Q.4b full wave bridge rectifier.

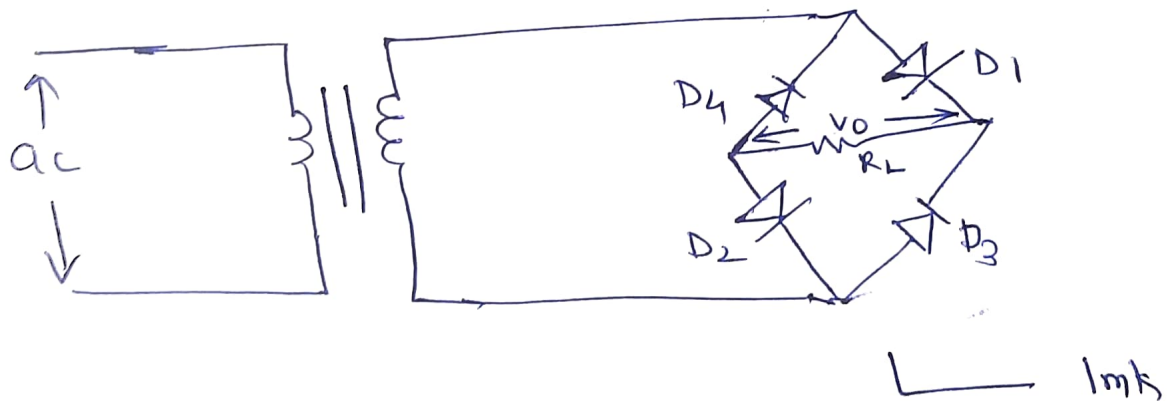

Step wise explanation ————— 4mks