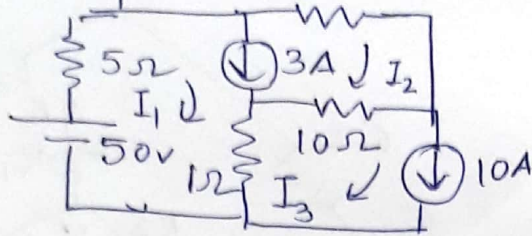


Q2 a)

Supernode,  $5\Omega$



mesh (1) & (2) forms

$$I_1 - I_2 = 3A \rightarrow [2M]$$

$$50 - 5I_1 - 5I_2 - 10(I_2 - I_3) - 1(I_1 - I_3) = 0$$

$$-6I_1 - 15I_2 + 11I_3 = -50$$

$$I_3 = 10 \rightarrow [1M]$$

$$\rightarrow [2M]$$

On solving the equations we get

$$I_1 = 9.76A$$

$$I_2 = 6.76A$$

$$I_3 = 10A$$


$$\rightarrow [2M]$$

Power delivered by voltage source =  $50I_1$  (01m)  
 $= 50 \times 9.76 = 488W$


$$I_{10\Omega} = I_3 - I_2 = 3.24A$$

$$(02m)$$

Q2 b)

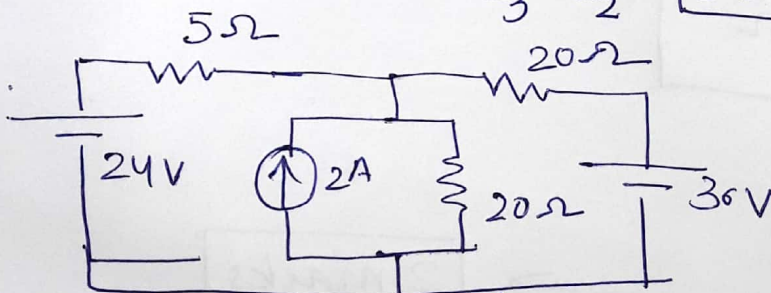

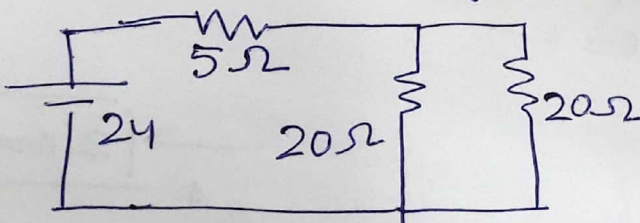
using Superposition theorem.  
 (1) Considering 24V only



$$I'_{5\Omega} = \frac{24}{5+10} = 1.6A \rightarrow$$

$$\rightarrow [3M]$$

(2) considering 2A acting alone.

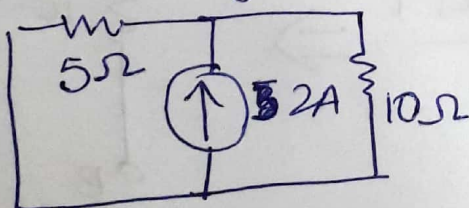


$$I''_{5\Omega} = \frac{2 \times 10}{5+10} = 1.33A \leftarrow$$

$$[3M]$$



(ii) Calculation of  $R_{th}$ .

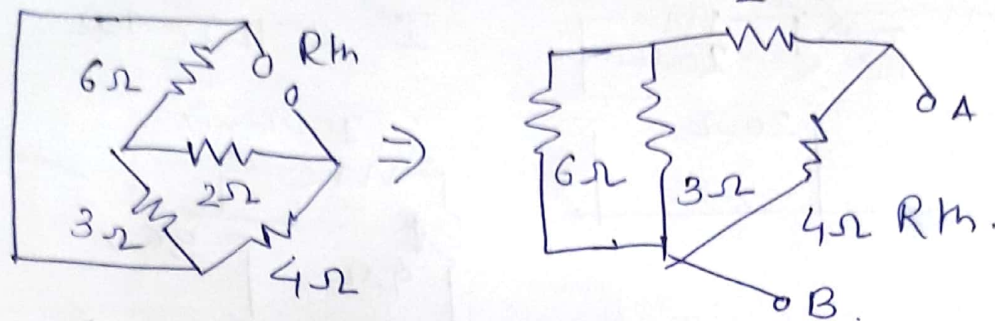

$$R_{th} = [(6 \parallel 3) + 2] \parallel 4 = 2\Omega$$

$$R_L = R_{th} = 2\Omega \rightarrow \boxed{4M}$$

(iii) Calculation of  $P_{max} = \frac{V_{th}^2}{4R_{th}} \rightarrow \boxed{450W}$

Q3(b). Solution

$$\begin{aligned} v &= V_m \sin \theta & 0 < \theta < \pi/4 \\ &= 0.707 V_m & \pi/4 < \theta < 3\pi/4 \\ &= V_m \sin \theta & 3\pi/4 < \theta < \pi \end{aligned} \quad (01)$$

(i) Average value  

$$V_{avg} = \frac{1}{\pi} \int_0^{\pi} v(\theta) d\theta$$

$$\begin{aligned} &= \frac{1}{\pi} \left[ \int_0^{\pi/4} V_m \sin \theta d\theta + \int_{\pi/4}^{3\pi/4} 0.707 V_m d\theta + \int_{3\pi/4}^{\pi} V_m \sin \theta d\theta \right] \\ &= \frac{V_m}{\pi} \left[ -\cos \theta \Big|_0^{\pi/4} + 0.707 \left[ \theta \right]_{\pi/4}^{3\pi/4} + \left[ -\cos \theta \right]_{3\pi/4}^{\pi} \right] \\ &= \frac{V_m}{\pi} (0.293 + 1.11 + 0.293) = \boxed{0.54 V_m} \end{aligned} \quad (03)$$

(ii) rms value of waveform


$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{\pi} \int_0^{\pi} v^2(\theta) d\theta} \\ &= \sqrt{\frac{1}{\pi} \left[ \int_0^{\pi/4} V_m^2 \sin^2 \theta d\theta + \int_{\pi/4}^{3\pi/4} (0.707 V_m)^2 d\theta + \int_{3\pi/4}^{\pi} V_m^2 \sin^2 \theta d\theta \right]} \\ &= \sqrt{\frac{V_m^2}{\pi} \left[ \left[ \frac{\theta}{2} - \frac{\sin 2\theta}{2} \right]_0^{\pi/4} + 0.499 \left[ \theta \right]_{\pi/4}^{3\pi/4} + \left[ \frac{\theta}{2} - \frac{\sin 2\theta}{4} \right]_{3\pi/4}^{\pi} \right]} \end{aligned} \quad (03)$$

$$= \sqrt{0.341 \text{ Vm}^2} = \boxed{0.584 \text{ Vm}}$$


iii) form factor =  $\frac{\text{Rms value}}{\text{Average value}} = \frac{0.584 \text{ Vm}}{0.54 \text{ Vm}} = 1.081$  (3m)

iv) Peak factor =  $\frac{\text{maximum value}}{\text{Rms value}} = \frac{1 \text{ Vm}}{0.584 \text{ Vm}} = 1.71$

Q.4  
(a)


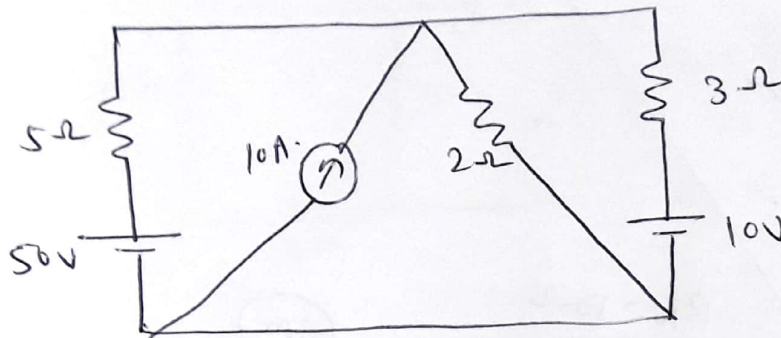


$$I_{5\Omega} = ?$$

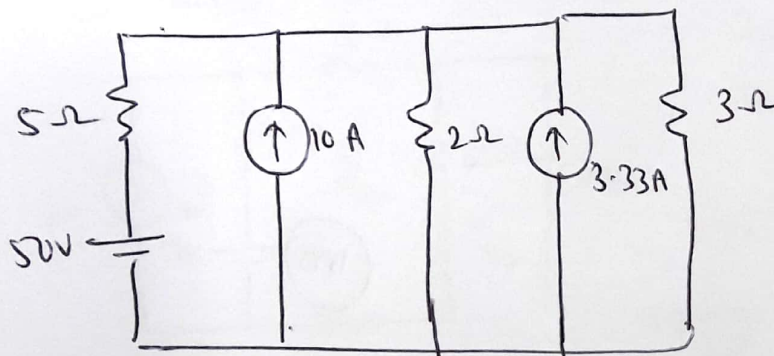

$$2 \text{ m}$$

1m

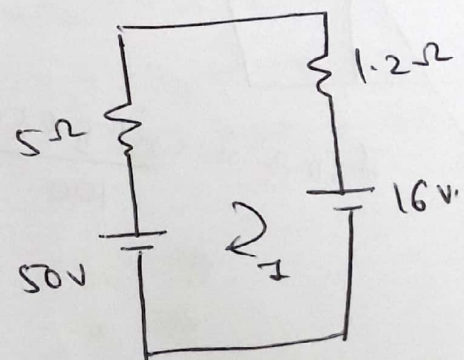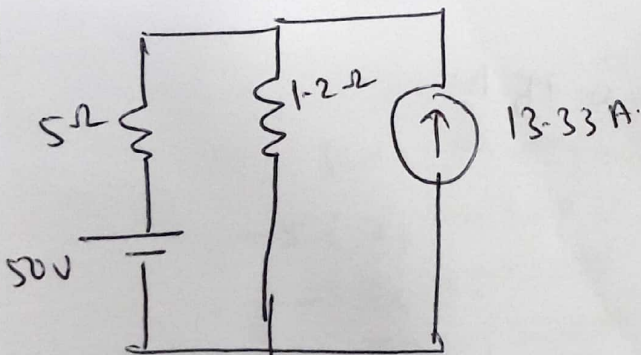

1m

$$50 - 5I - 1.2I - 16 = 0$$


$$I = 5.48 \text{ A (A)}$$

1m




Nortons.

Q.416)

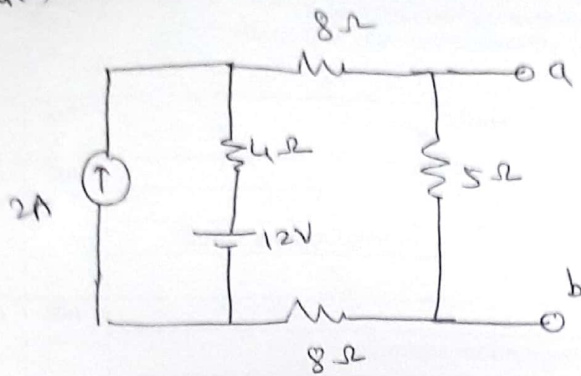

$$R_L = 50\Omega$$

To find  $R_N$ .

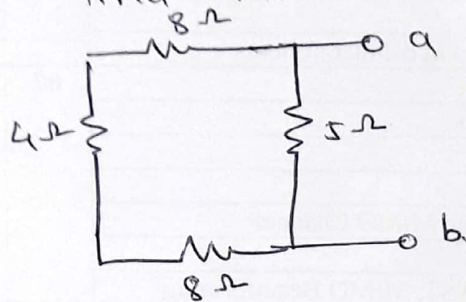


$$R_N = (8 + 4 + 8) \parallel 5$$

$$= 20 \parallel 5$$

$$R_N = 4\Omega$$

(1m)

To find  $I_N$ .

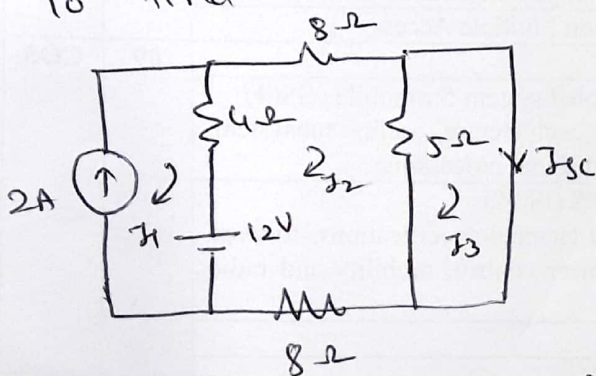

$$I_3 = I_{sc}$$

$$I_1 = 2A$$

KVL to loop II

$$12 - 4(I_2 - I_1) - 8I_2 - 5(I_2 - I_3) = 0$$

$$12 - 4I_2 + 4I_1 - 8I_2 + 5I_2 + 5I_3 - 5I_2 = 0$$

$$4I_1 - 7I_2 + 5I_3 = -12$$

$$-5I_2 + 5I_3 = -20$$

— (1)

KVL to loop III

$$-5(I_3 - I_2) = 0$$


$$-5I_3 + 5I_2 = 0$$

$$5I_2 - 5I_3 = 0$$

$$I_2 = I_3$$


$$I_3 = 1A$$

— (2m)

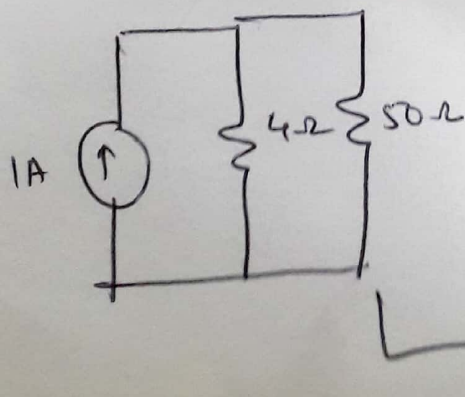


$$I_{50\Omega} = \frac{1 \times 4}{54} = 0.0740 \text{ Amp.}$$

— (1m)

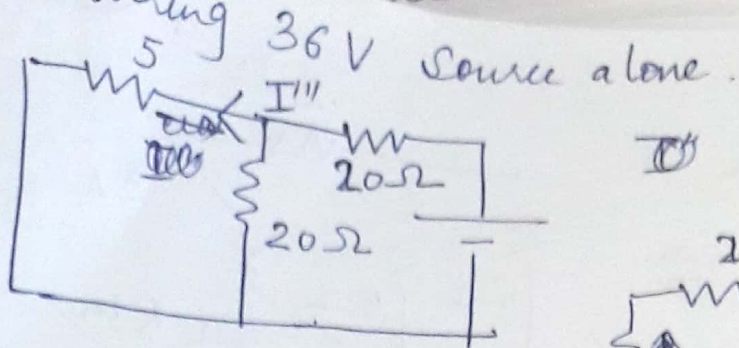

$20 || 5 = 4\Omega$

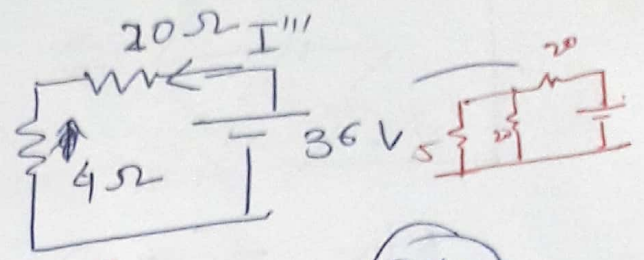

$$I''' = \frac{36}{4+20} = \frac{36}{24} = (1.5A) \leftarrow$$

$I_{5\Omega} = \frac{1.5 \times 20}{25} = 1.2A (\leftarrow)$

3M


By superposition theorem

$$I_{5\Omega} = I'_{5\Omega} + I''_{5\Omega} + I'''_{5\Omega}$$

$$= 1.6(\rightarrow) + 1.33(\leftarrow) + 1.5(\leftarrow) = 0.933A (\leftarrow)$$

$$= 1.23A (\leftarrow) \rightarrow 1M$$

Q3 a)

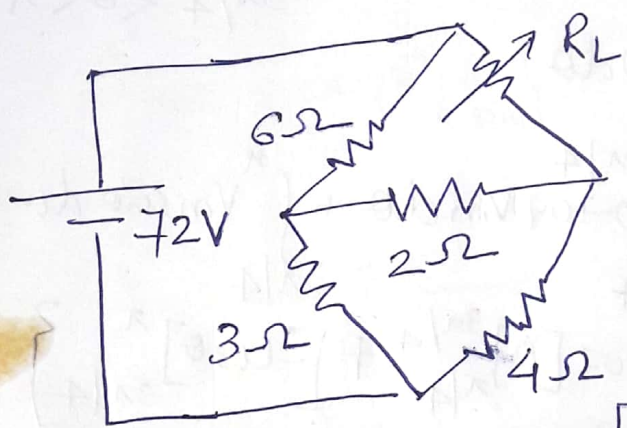

① Calculation of  $V_{th}$   
KVL at mesh 1

$$72 - 6I_1 - 3(I_1 - I_2) = 0$$


$$9I_1 - 3I_2 = 72$$

KVL at mesh 2

$$-3(I_2 - I_1) - 2I_2 - 4I_2 = 0$$

$$-3I_1 + 1I_2 = 0$$

$I_1 = 9A, I_2 = 3A$

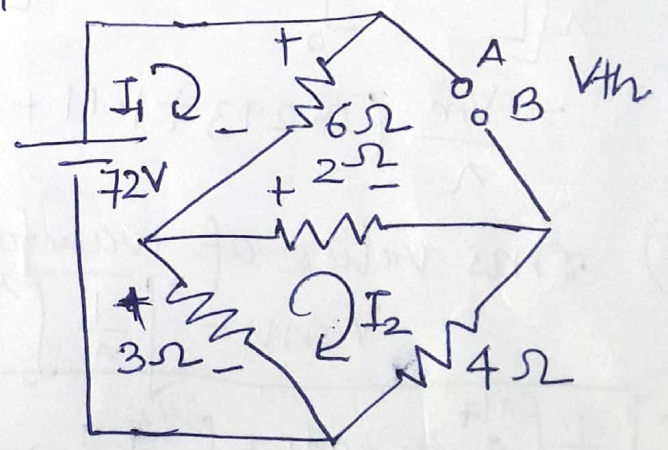



$$V_{th} - 6I_1 - 2I_2 = 0$$

$$= 60V \rightarrow 4M$$





# Solution & Scheme

Q1)

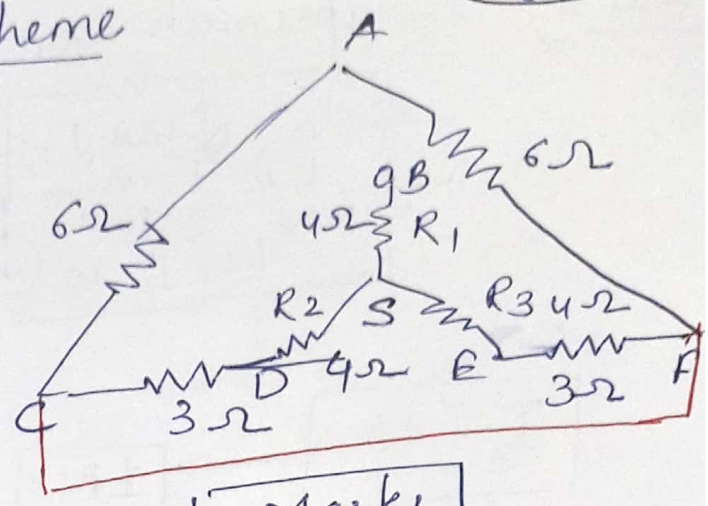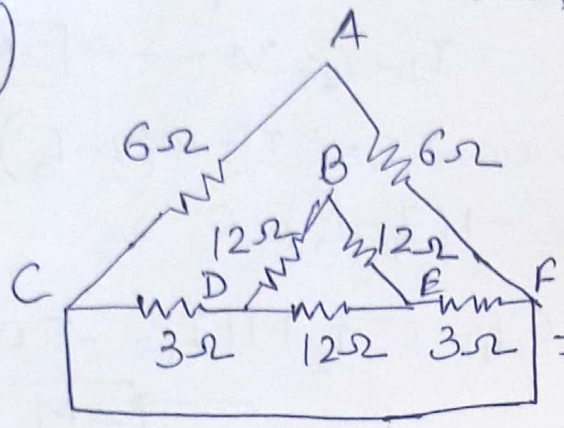

$$R_1 = R_2 = R_3 = \frac{12 \times 12}{12 + 12 + 12} = 4\Omega \rightarrow \boxed{12 \text{ Marks}}$$

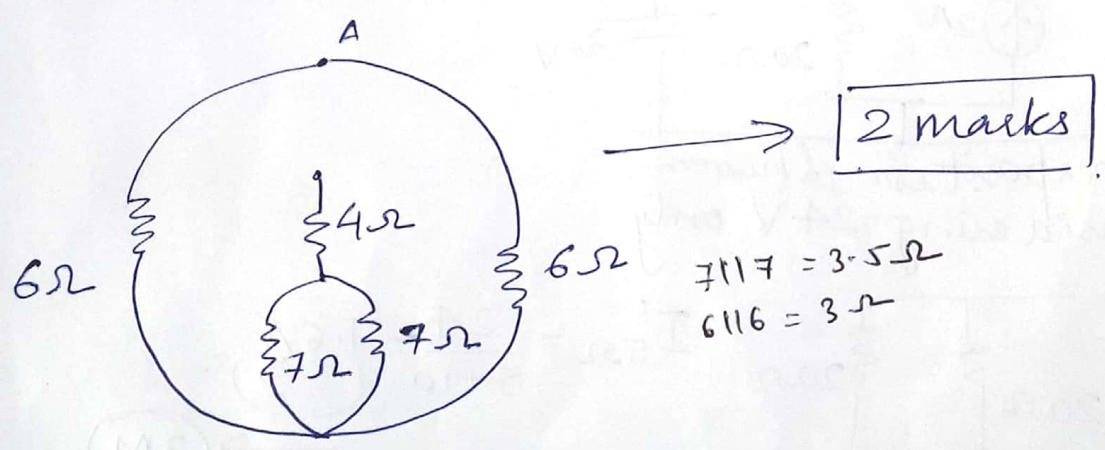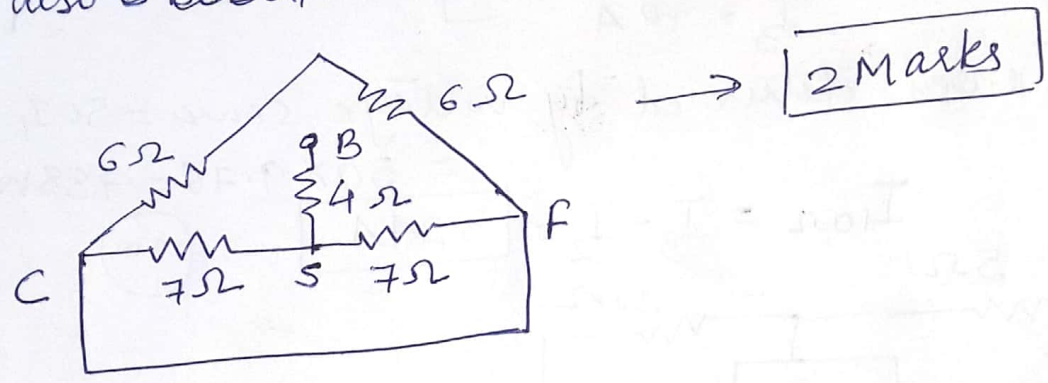In branch CDS  $3\Omega$  &  $4\Omega$  in series  
also  $4\Omega$  &  $3\Omega$  in series



$$\begin{aligned} 7 \parallel 7 &= 3.5\Omega \\ 6 \parallel 6 &= 3\Omega \end{aligned}$$

