


Ques  
. No.

Q. 1

Solve Any two of the following

(a) Find the current in  $1\ \Omega$  resistor using nodal analysis.

Mark

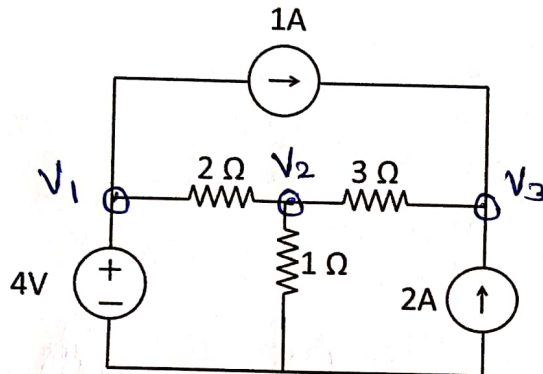

Using Nodal Analysis

$$V_1 = 4V \quad \text{--- (1)}$$

KCL at node (2)

$$\frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_2 - V_3}{3} = 0$$

$$-3V_1 + 11V_2 - 2V_3 = 0$$

$$11V_2 - 2V_3 = 12 \quad \text{--- (A)}$$

KCL at node (3)



$$\frac{V_3 - V_2}{3} = 2 + 1$$

$$-V_2 + V_3 = 9 \quad \text{--- (B)}$$

solving (A) & (B)  $V_2 = \frac{30}{9} = 3.33V$

$$I_{1\Omega} = \frac{V_2}{1} = \frac{3.33}{1} = 3.33A \quad \text{--- (2)}$$

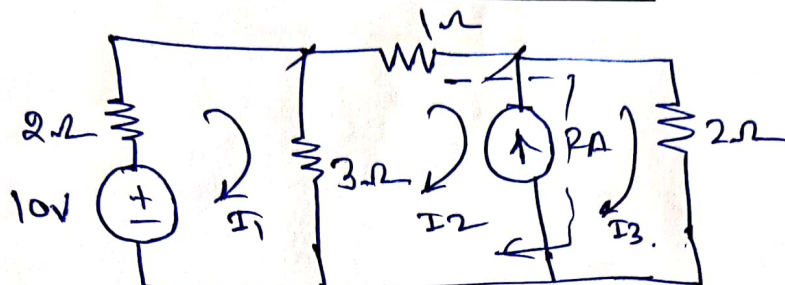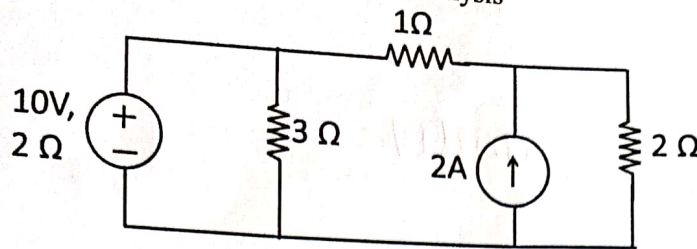(b) Find current in  $2\ \Omega$  resistor using mesh analysis



KVL to mesh ①

$$10 - 2I_1 - 3(I_1 - I_2) = 0$$

$$5I_1 - 3I_2 = 10 \quad \text{--- (1)} \quad \text{--- (2)}$$

2A Current source on Common Branch of mesh ② & ③ so super mesh.

KVL to super mesh

$$I_2 + 2 = I_3 \quad \text{---}$$

$$I_2 - I_3 = -2 \quad \text{--- (11) (2)}$$

$$-3(I_2 - I_1) - I_2 - 2I_3 = 0$$

$$-3I_2 + 3I_1 - I_2 - 2I_3 = 0$$

$$\cancel{2I_1} - \cancel{3I_2}$$


$$+ 3I_1 - 4I_2 - 2I_3 = 0 \quad \text{--- (11') (3)}$$

solving ① ⑪ & ⑪'  $I_1 = \frac{16}{3}, I_2 = \frac{10}{3}$


$$\boxed{I_3 = 2.476\text{A}} \quad \text{--- (3)}$$



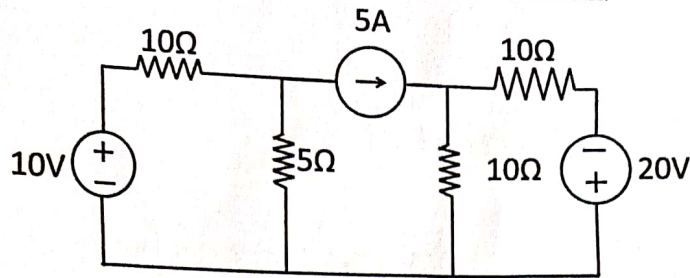(c) Find voltage across  $5\Omega$  resistor using Thevenin's theorem.



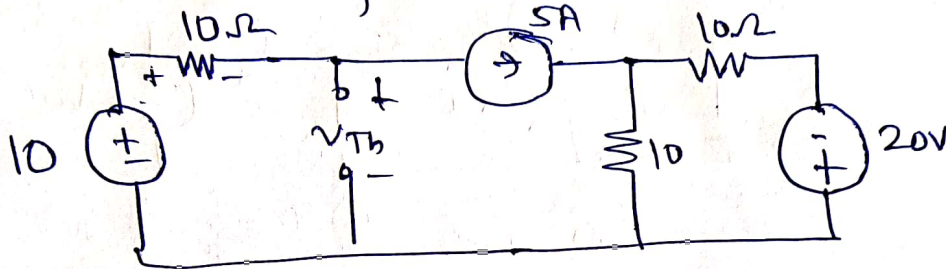$\Rightarrow$  Remove load & find  $V_{Th}$ .




$$V_{10\Omega} = 10 \times 5 = 50V$$

$$V_{Th} = -50 + 10 = -40V.$$

--- (4)


$\Rightarrow$  To find  $R_{Th}$ .

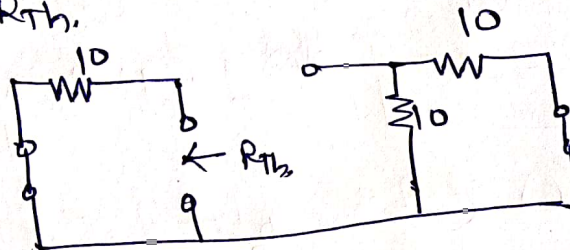

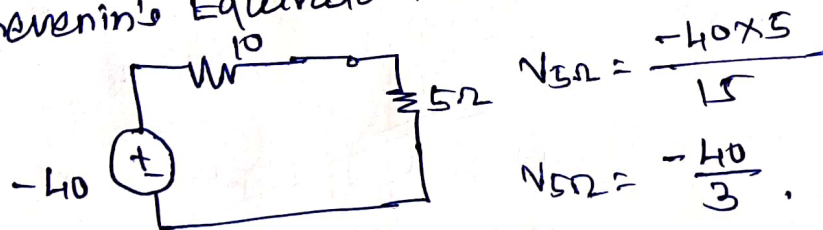--- (3)

$$\underline{R_{Th} = 10\Omega}$$

$\Rightarrow$  Thevenin's Equivalent Circuit



$$V_{5\Omega} = \frac{-40 \times 5}{15}$$


$$V_{5\Omega} = -\frac{40}{3}$$

--- (3)

$$\boxed{V_{5\Omega} = -13.33V}$$

Q. 2

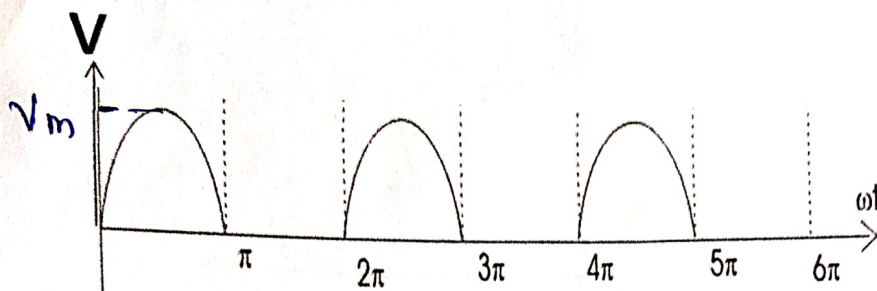(a) Find RMS value of the following waveform.



$$\Rightarrow V_{rms} = \left[ \frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega t)^2 d\omega t \right]^{1/2} \quad \text{--- (2)}$$

$$= \left[ \frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t d\omega t \right]^{1/2}$$

$$= \left[ \frac{1}{2\pi} V_m^2 \int_0^{\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{2\pi} \cdot \frac{1}{2} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi} \right]^{1/2}$$

$$= \left[ \frac{V_m^2}{4\pi} \left[ \pi - \frac{\sin 2\pi}{2} - 0 + \sin 0 \right] \right]^{1/2}$$


$$= \left[ \frac{V_m^2}{4\pi} (\pi) \right]^{1/2}$$

$$V_{rms} = \left[ \frac{V_m}{2} \right]$$

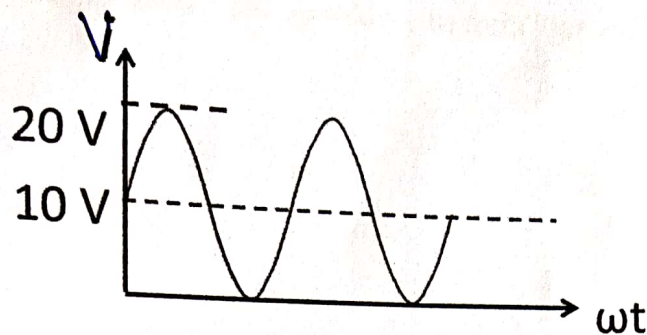(4)



Find average value of the following waveform.



$$V = 10 + 10 \sin \omega t \quad \dots \quad (2)$$

$$\begin{aligned} V_{av} &= \frac{1}{2\pi} \int_0^{2\pi} (10 + 10 \sin \omega t) d\omega t \\ &= \frac{1}{2\pi} \left[ 10\omega t + 10 \cos \omega t \right]_0^{2\pi} \\ &= \frac{1}{2\pi} \left[ 10 \times 2\pi - 10 \cos 2\pi - 0 + 10 \cos 0 \right] \\ &= \frac{1}{2\pi} \left[ 2\pi \times 10 - 1 + 1 \right] \end{aligned}$$


$$V_{av} = 10V.$$

(4)

Q. 3

Solve any two of the following

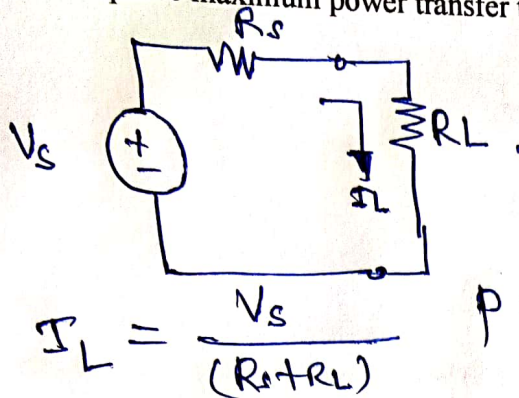(a) State and prove maximum power transfer theorem.




statement (1)

$$P = I_L^2 \cdot R_L = \left( \frac{V_s^2}{(R_s + R_L)^2} \right) \cdot R_L \quad (1)$$

$$\frac{dP}{dR_L} = 0 \quad \frac{dP}{dR_L} = \frac{d}{dR_L} \left( \frac{V_s^2 R_L}{(R_s + R_L)^2} \right) \quad \text{Solving} \quad (1)$$

$$\boxed{R_s = R_L} \quad \text{and} \quad P_{max} = \frac{V_s^2}{4R_L}$$

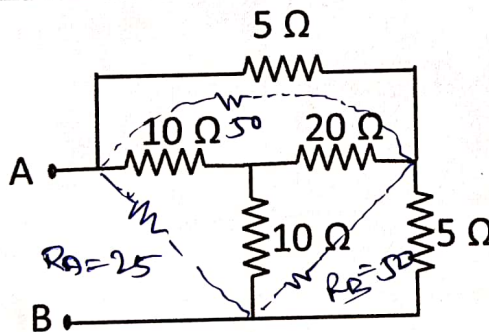(b) Find resistance between terminals A and B.



$$\Sigma R = 10 \times 20 + 20 \times 10 + 10 \times 10$$



$$\Sigma R = 200 + 200 + 100$$

$$\Sigma R = 500$$


$$R_B = \frac{500}{10} = 50 \Omega \quad (2)$$

$$R_A = \frac{500}{20} = 25$$

$$R_C = \frac{500}{10} = 50 \Omega$$

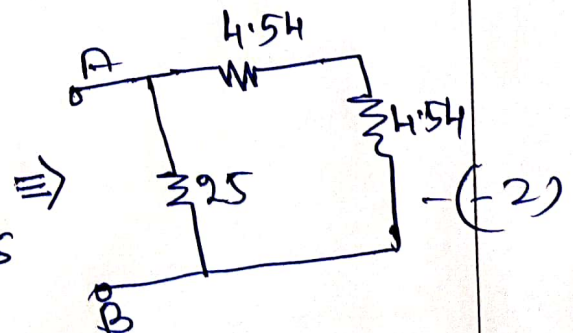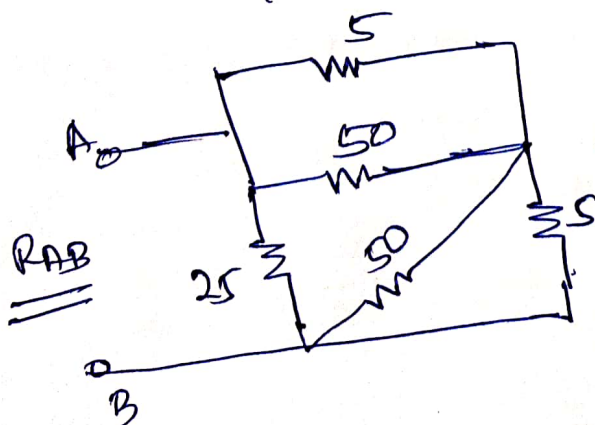





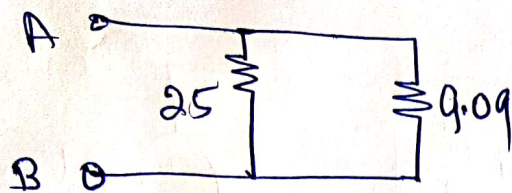


$$R_{AB} = 6.66 \Omega$$

(1)

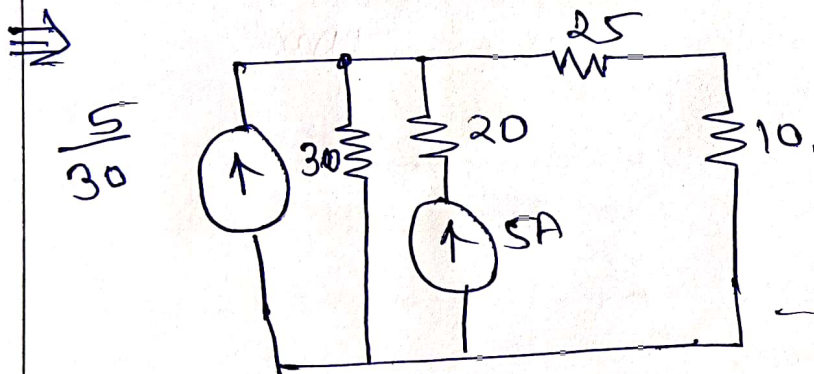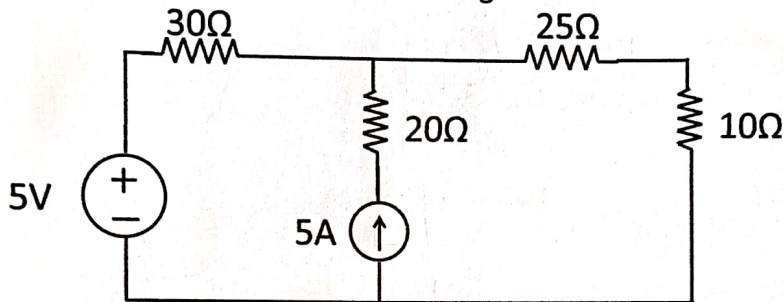(c) Find the current in  $10 \Omega$  resistor using source transformations.



(2)

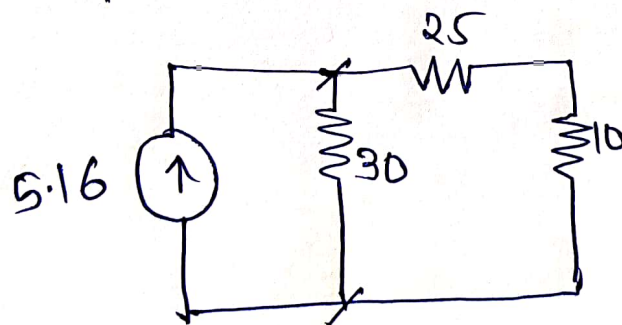

(2)

using Current Division Rule

$$I_{10\Omega} = \frac{5.16 \times 30}{30 + 25 + 10} = \frac{155}{65}$$

$$I_{10\Omega} = 2.384 A$$

(1)