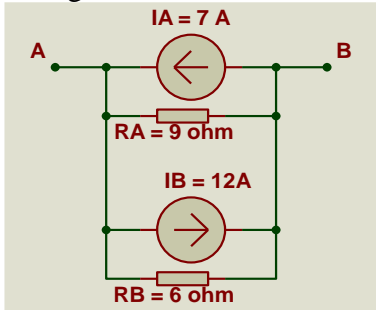
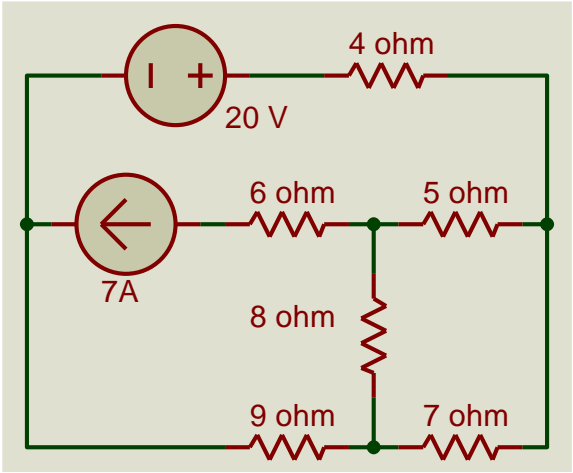
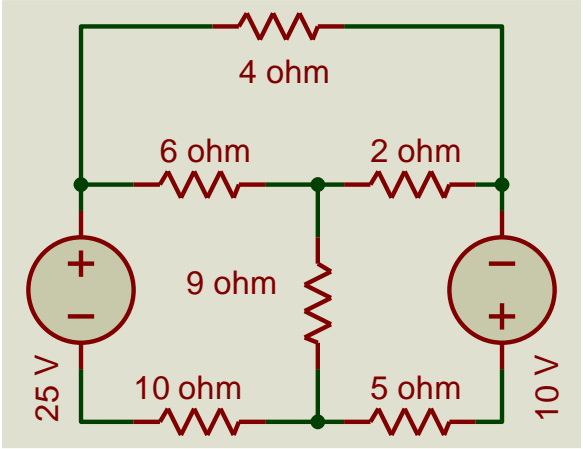


Semester: October 2021 – February 2022 Examination: ESE Examination		
Programme code: 01 Programme: B. TECH	Class: FY/SY/TY/LY	Semester: I/H/II/IV/V/VI/VII/VIII (SVU 2020)
Name of the Constituent College: K. J. Somaiya College of Engineering	Name of the Department COMP/IT/MECH	
Course Code: 116U06C107	Name of the Course: Element of Electrical & Electronics Engineering	
Duration : 1 Hour 45 Minutes (15 minutes extra for uploading)	Maximum Marks : 50	
Instructions: 1)Draw neat diagrams 2) Assume suitable data if necessary		

Q. No.		Max Marks
Q1 (A)	<p>I. If two current sources I_A (7A and internal resistance of $9\ \Omega$) and I_B (12A and internal resistance of $6\ \Omega$) are connected as shown below, then equivalent voltage source between terminal A & B will be ____.</p>  <p> A. $V_{AB} = -18V, 3.6\ \Omega$ B. $V_{AB} = +18V, 3.6\ \Omega$ C. $V_{AB} = -45V, 15\ \Omega$ D. $V_{AB} = +45V, 15\ \Omega$ </p> <p>II. In a OP-AMP based inverting amplifier, if feedback gain is 4 and input signal is 2V peak to peak AC, then output is ____.</p> <p> A. 8V peak to peak and in phase with input signal B. 8V peak and out of phase with input signal C. 8V peak and in phase with input signal D. 8V peak to peak and out of phase with input signal </p> <p>III. In a Zener diode, if breakdown voltage is high, then ____.</p> <p> A. both P and N are heavily doped B. P-type is heavily doped and N-type is lightly doped C. both P and N are lightly doped D. P-type is lightly doped and N-type is heavily doped </p> <p>IV. If line voltage of 450 V, is supplied to 3Φ star type balanced network of pure resistance $15\ \Omega$/phase, then line current will be ____A.</p> <p> A. 10 B. 51.96 C. 30 D. 17.32 </p>	10

	<p>V. Which DC motor is most suitable for elevators?</p> <p>A. DC cumulative compound motor B. DC differential compound motor C. DC series motor D. DC shunt motor</p> <p>VI. A circuit with a resistor, inductor and capacitor in series is resonant of f_0 Hz. If all the component values are now doubled, the new resonant frequency is.</p> <p>A. $2f_0$ B. $f_0/4$ C. $f_0/2$ D. f_0</p> <p>VII. If each branch of a delta network has resistance $18\ \Omega$, then each branch of the equivalent star type network has resistance $__\ \Omega$.</p> <p>A. 3 B. 6 C. 9 D. 54</p> <p>VIII. A parallel resonant circuit consists of iron core coil of $R\ \Omega$ resistance and L H inductance in parallel with capacitor of $C\ \mu\text{F}$, behaves like $__\$.</p> <p>A. a pure resistor of value much higher than R B. a pure resistor of value R C. an open circuit D. a short circuit</p> <p>IX. In the two wattmeter method of measurement, if wattmeter readings are equal and opposite, then phase angle of the load is $____\$.</p> <p>A. 60° B. 90° C. 0° D. 30°</p> <p>X. The inductive reactance of a 1Φ transformer depends on $__________\$.</p> <p>A. EMF B. MMF C. magnetic flux D. leakage flux</p>	
Q1 (B)	<p>Attempt any FIVE questions out of the following SEVEN questions.</p> <p>I. Convert star network of $R_A=8\ \Omega$, $R_B=11\ \Omega$ & $R_C=15\ \Omega$ to equivalent delta network.</p> <p>II. What is addition of $I_1 = 20\sin(\omega t + \frac{\pi}{4})$, $I_2 = 14\sin(\omega t - \frac{\pi}{6})$?</p> <p>III. Draw input and output characteristics of a common-emitter amplifier.</p> <p>IV. What are advantages of Zener diode?</p> <p>V. Define superposition theorem.</p> <p>VI. A load resistance ($R_L\ \Omega$) is connected across 15V DC supply with internal resistance of $16\ \Omega$. What is the maximum power that can be absorbed by the load resistance?</p> <p>VII. Compute quality factor in a parallel R-L-C resonant circuit where $R=9\ \Omega$, $L=0.12\ \text{H}$ and $C=330\ \mu\text{F}$.</p>	10

Q. 2	<p>Attempt any two questions</p> <p>I. Draw phasor diagram of single phase transformer considering its winding resistance and magnetic leakages, when capacitive load is connected to it.</p> <p>II. Two wattmeters are used to measure input power of a 3Φ balanced delta circuit consisting of impedance $(15+j10) \Omega$. If supply voltage is 400V, 3Φ AC then calculate readings of both the wattmeters.</p> <p>III. Draw neat circuit diagram of a single phase bridge rectifier and explain its working.</p>	10
Q. 3	<p>Calculate power absorbed in 9Ω resistor in the following circuit using mesh analysis method.</p>  <p style="text-align: center;">OR</p> <p>Calculate current flowing through 4Ω resistor in the following circuit using Norton's theorem.</p> 	10
Q. 4	<p>An iron core coil is connected across a non-inductive resistance of 80Ω. When a 240 V, 50 Hz, 1Φ AC supply is connected to the circuit, the coil draws current of 5 A and total circuit current is 7 A. Determine self-resistance and inductance of the coil, power absorbed by the coil and total power absorbed by the circuit.</p>	10