
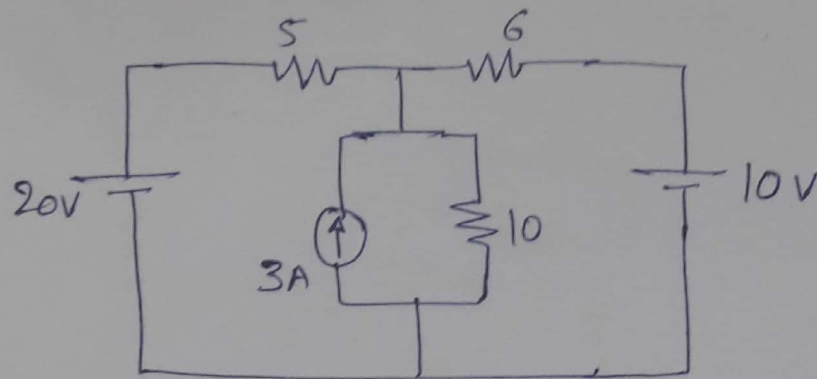


Q1. SPT $I_{5\Omega} = ?$

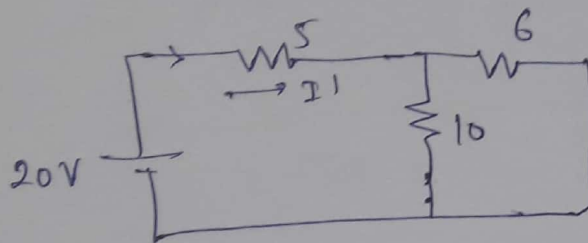

Soln: i) Consider 20V source only:




using CDR

$$I' = \frac{20}{5 + (6 \parallel 10)} = \frac{20}{5 + 3.75}$$

$$I' = 2.286 \text{ A } (\rightarrow)$$

02M

ii) Consider 3A source only:

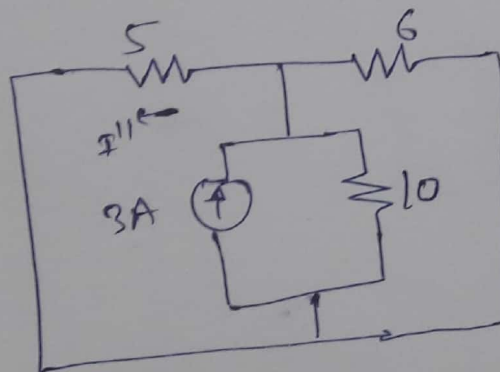


using CDR

$$I'' = \frac{3 \times (10 \parallel 6)}{5 + 3.75}$$

$$I'' = 1.286 \text{ A } (\leftarrow)$$

02M

iii) Consider 10V source only:

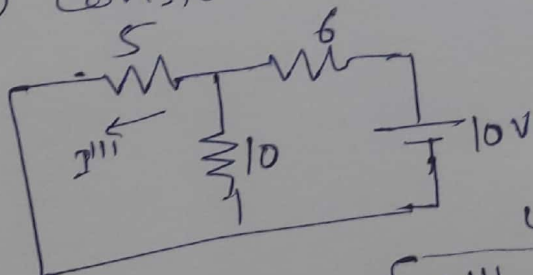

$$I_T = \frac{10}{6 + (5 \parallel 10)} = \frac{10}{3.33 + 6}$$

$$\Rightarrow I_T = 1.0718 \text{ A}$$

using CDR:

$$I''' = \frac{1.0718 \times 10}{10 + 5} = 0.714 \text{ A } (\leftarrow)$$

02M



using SPT:

$$I_{5\Omega} = I' - I'' - I'''$$

$$= 2.286 - 1.286 - 0.714 = 0.286 \text{ A } (\rightarrow)$$

01M

Q2

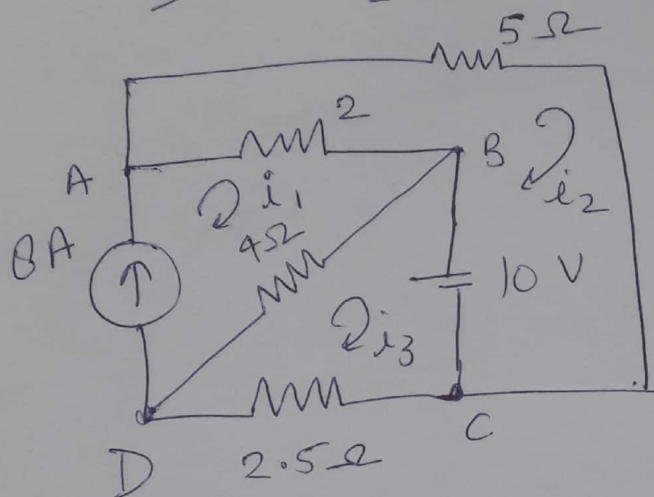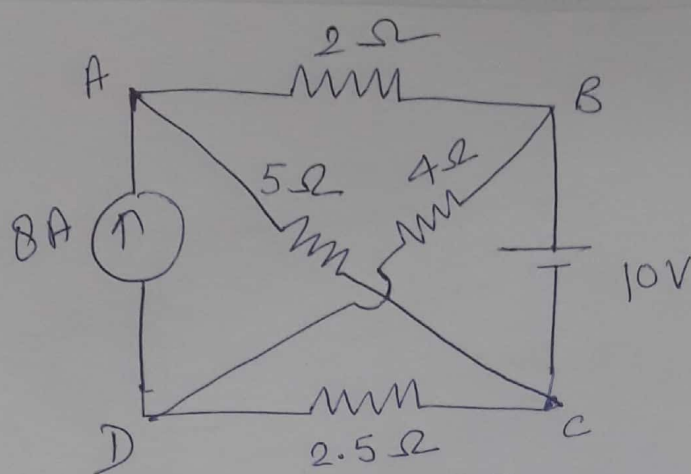

$$i_1 = 8A$$

Loop 1; $-2(8-i_2) - 4(8-i_3) = 0$

$$2i_2 + 4i_3 = 48 \quad \text{--- 2M}$$

Loop 2; $-2(i_2-8) - 5i_2 + 10 = 0$

$$-7i_2 = -26$$

$$i_2 = \frac{26}{7} = 3.714A \quad \text{--- 2M}$$

Loop 3; $-4(i_3-8) - 10 - 2.5i_3 = 0$

$$-6.5i_3 = -22 \quad \text{--- 2M}$$

$$i_3 = 3.384A$$

$$I_{2\Omega} = i_1 - i_2 = 8 - 3.714 = 4.286A$$


$$I_{5\Omega} = i_2 = 3.714A$$

$$I_{4\Omega} = i_1 - i_3 = 8 - 3.384 = 4.615A$$

$$I_{2.5\Omega} = i_3 = 3.384A$$

4M

Q2 (OR)

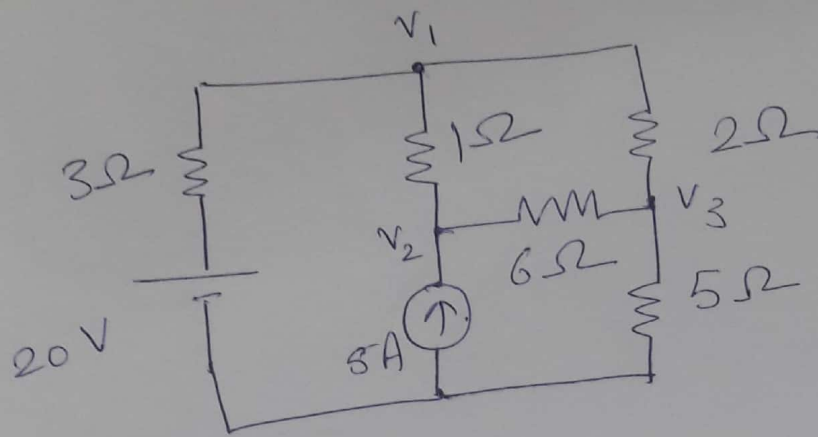

KCL at node 1

$$\frac{V_1 - 20}{3} + \frac{V_1 - V_2}{1} + \frac{V_1 - V_3}{2} = 0$$

$$\Rightarrow 1.83 V_1 - V_2 - 0.5 V_3 = 6.67 \quad \text{--- (1)}$$

KCL at node 2

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{6} = 5$$

$$-V_1 + 1.17 V_2 - 0.17 V_3 = 5 \quad \text{--- (2)}$$

KCL at node 3

$$\frac{V_3 - V_2}{6} + \frac{V_3}{5} + \frac{V_3 - V_2}{6} = 0$$

$$-0.5 V_1 - 0.17 V_2 + 0.87 V_3 = 0 \quad \text{--- (3)}$$

Solving (1), (2), (3) \Rightarrow



$$V_1 = 23.82 \text{ V}$$

$$V_2 = 27.4 \text{ V}$$

$$V_3 = 19.04 \text{ V}$$

$$I_{6\Omega} = \frac{V_2 - V_3}{6} = \frac{27.4 - 19.04}{6} = 1.39 \text{ A}$$


Q3

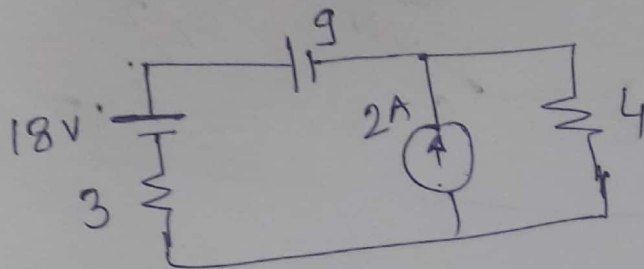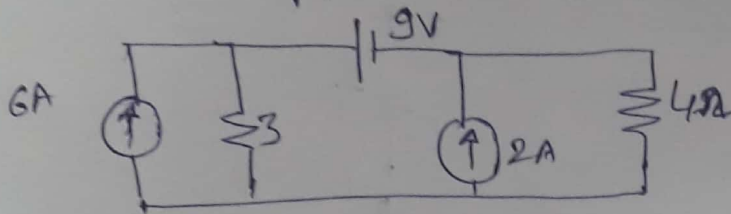Find current thro' 4Ω resist.



Combining 9V & 18V

0.2M

0.1M

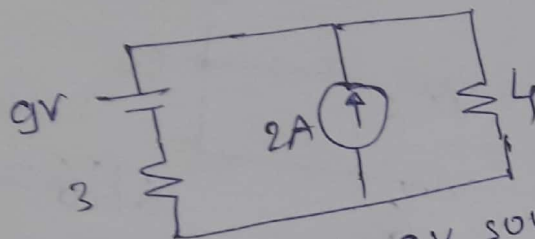

convert 9V source into E-S

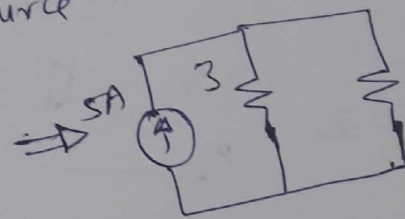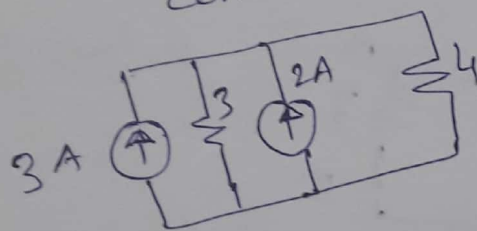


0.2M

0.1M

$$I_{4\Omega} = \frac{5 \times 3}{7} = \frac{15}{7} = \underline{\underline{2.143 \text{ A}}}$$

OK



Q3

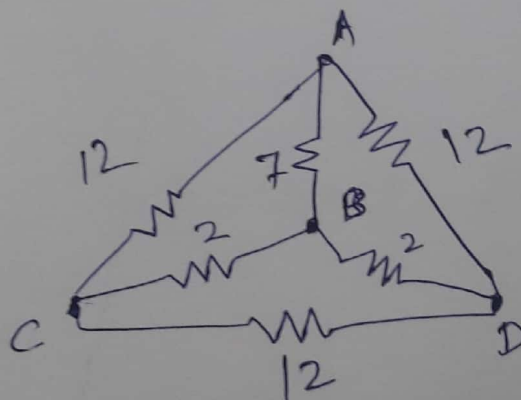 $R_{AB} = ?$


Converting outer Delta ACD into star.

Page 4

P.T.O.

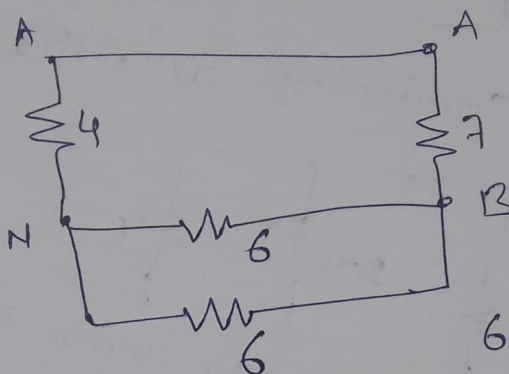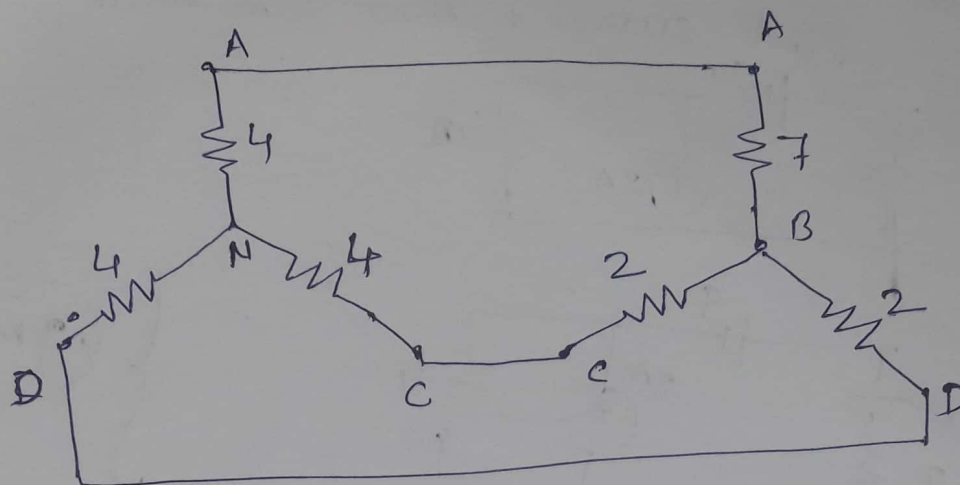

$$6 \parallel 6 = 3\Omega$$

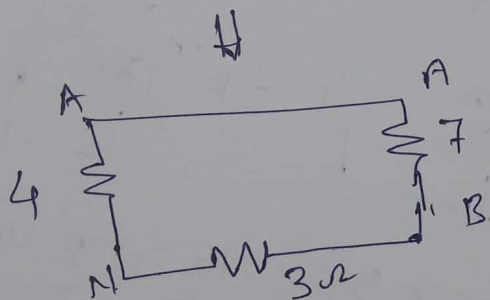

$$R_{AB} = 7 \parallel 7 = 3.5\Omega$$

Page 5

Sol 4:- Given $v = 325 \sin 314t$

$$v = V_m \sin \omega t$$

$$V_m = 325 \text{ volt}$$

$$\text{RMS value } V_{(RMS)} = \frac{V_m}{\sqrt{2}} = \frac{325}{1.414} = 230 \text{ V}$$

$$\omega = 314$$

$$2\pi f = 314$$

$$\Rightarrow f = 50 \text{ Hz}$$

$$\text{Now } i = 14.14 \sin(314t - 60^\circ)$$

$$\text{comparing } i = I_m \sin(\omega t - \phi)$$

$$\Rightarrow I_m = 14.14$$

$$\text{RMS value } I_{(RMS)} = \frac{I_m}{\sqrt{2}} = \frac{14.14}{1.414} = 10 \text{ Amp.}$$

$$\text{Power factor Angle } \phi = 60^\circ$$

$$\text{Power factor, } \cos \phi = \cos 60^\circ = 0.5 \text{ lagging}$$

$$\text{Power consumed } P = VI \cos \phi$$

$$= 230 \times 10 \times 0.5$$

$$= 1150 \text{ watts}$$

$$\text{Impedance } Z = \frac{V}{I} = \frac{230 \angle 0^\circ}{10 \angle -60^\circ}$$

$$= 23 \angle 60^\circ \Omega$$

$$\begin{aligned} \text{In complex form } Z &= 23(\cos 60^\circ + j \sin 60^\circ) \\ &= 23 \times 0.5 + j 23 \times 0.866 \\ &= 11.5 + j 19.918 \Omega \end{aligned}$$

$$Z = R + jX_L$$


$$\Rightarrow R = 11.5 \Omega$$

$$X_L = \frac{19.918}{22.99} \Omega$$

$$\omega L = 22.99 \times 19.918 \Omega$$


$$2\pi fL = 22.99 \times 19.918 \Omega$$
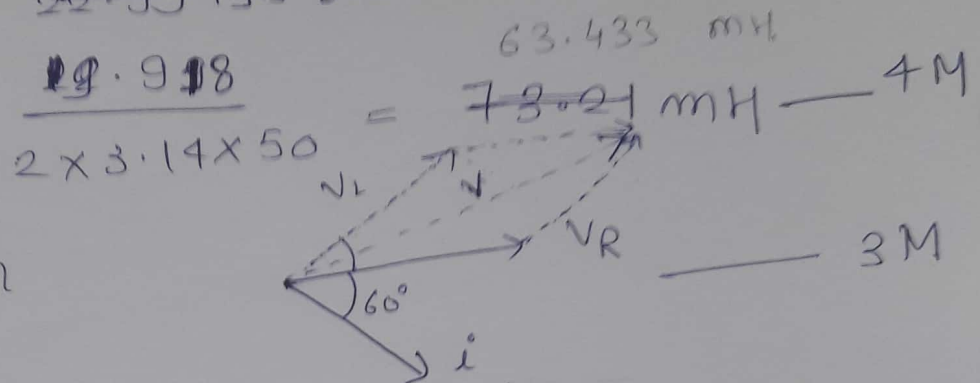
$$\Rightarrow L = \frac{19.918}{2 \times 3.14 \times 50}$$



Phasor

Sol:-

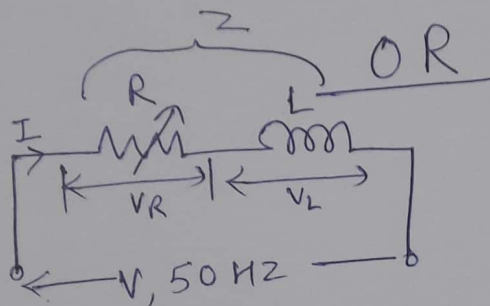

Given $L = 100 \text{ mH}$

$$X_L = \omega L = 2\pi fL = 2 \times 3.14 \times 50 \times 100 \times 10^{-3}$$

$$= 31.4 \Omega$$

condition is $V_L = \frac{1}{2} V$ — 2M

$$V_L = I X_L$$

$$V = I Z = I \sqrt{R^2 + X_L^2}$$

$$V_L = \frac{V}{2}$$

$$I X_L = \frac{I \sqrt{R^2 + X_L^2}}{2}$$

$$\Rightarrow \sqrt{R^2 + X_L^2} = 2 X_L = 2 \times 31.4 \Omega$$

$$= 62.8 \Omega$$

Page 2

$$R^2 + X_L^2 = (62.8)^2$$

$$R^2 = (62.8)^2 - (31.4)^2$$

$$R^2 = 3943.8 - 985.9$$

$$\Rightarrow R = 54.4 \Omega$$

8 M

page 8

Q5:

$$v(t) = \begin{cases} \frac{30}{T} t, & 0 < t < T/3 \\ 10V, & T/3 < t < 2T/3 \\ -\frac{30}{T} t + 30, & 2T/3 < t < T \end{cases} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{01M}$$

(i) V_{avg} = $\frac{1}{T} \int_0^T v(t) \cdot dt$

$$V_{avg} = \frac{1}{T} \left[\int_0^{T/3} \frac{30t}{T} dt + \int_{T/3}^{2T/3} 10 \cdot dt + \int_{2T/3}^T \left(-\frac{30t}{T} + 30\right) dt \right] \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{02M}$$

By solving:

$$\boxed{V_{avg} = 6.33 V}$$

(ii) V_{rms} = $\sqrt{\frac{1}{T} \int_0^T v(t)^2 \cdot dt}$

$$= \sqrt{\frac{1}{T} \left[\int_0^{T/3} \left(\frac{30t}{T}\right)^2 dt + \int_{T/3}^{2T/3} 10^2 \cdot dt + \int_{2T/3}^T \left(-\frac{30t}{T} + 30\right)^2 dt \right]} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{03M}$$

By solving:-

$$\Rightarrow \boxed{V_{rms} = 7.45 V}$$

(a) Form factor = $\frac{\text{RMS value}}{\text{Average value}}$

(b) Peak/Crest Factor = $\frac{\text{Peak value}}{\text{RMS value}}$

} 02.

SL.

Megha Sharma
BTRX

(Mus Swider Raut)
EXTC