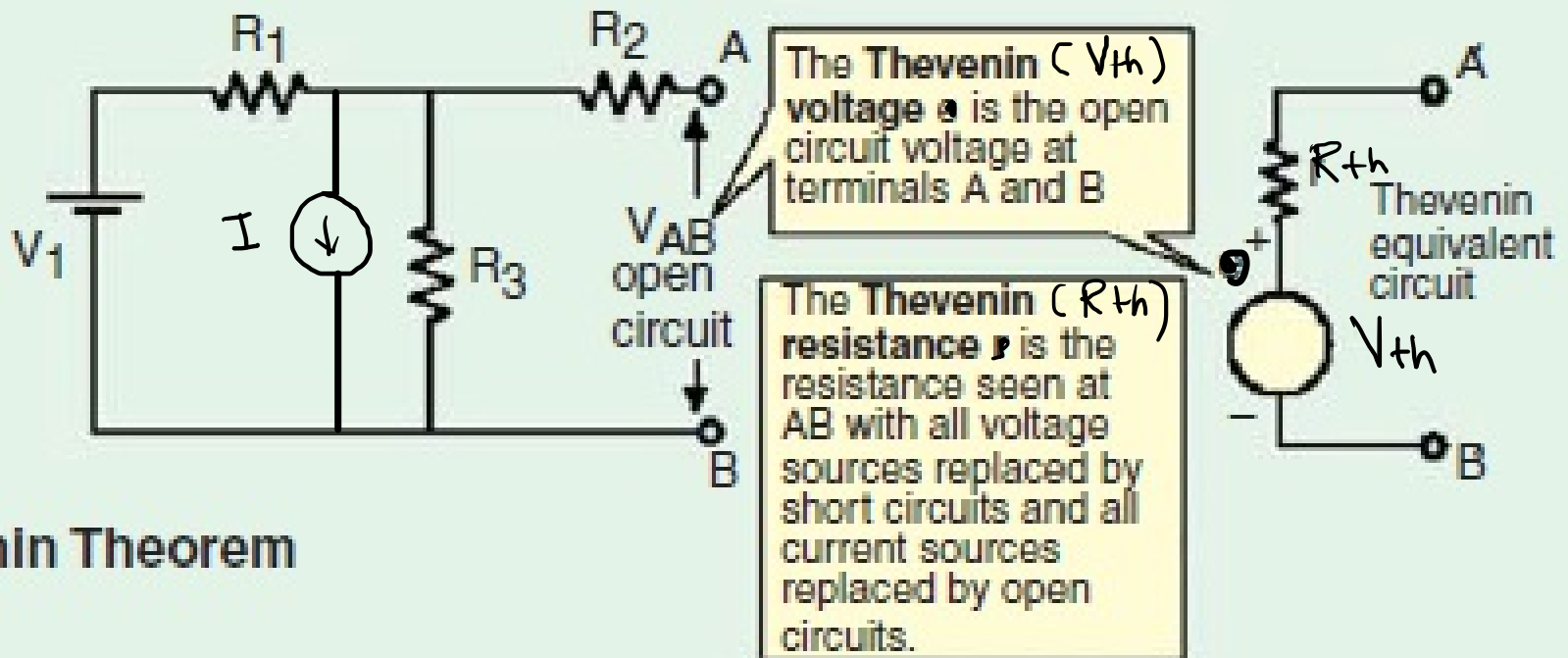


Thevenin's Theorem

Statement:


Any linear, active bilateral network can be replaced by a voltage source (V_{th}) in series with a resistance (R_{th}) where V_{th} is the open-circuit voltage (i.e. voltage across the two terminals when R_L is removed) and R_{th} is the internal resistance of the network as viewed back into the open-circuited network from terminals A and B with all energy sources replaced by their internal resistance. (Ideal current sources by infinite resistance and Ideal voltage source by zero resistance).




Thevenin's Theorem

Steps to analyse network using Thevenin's Theorem

Given network

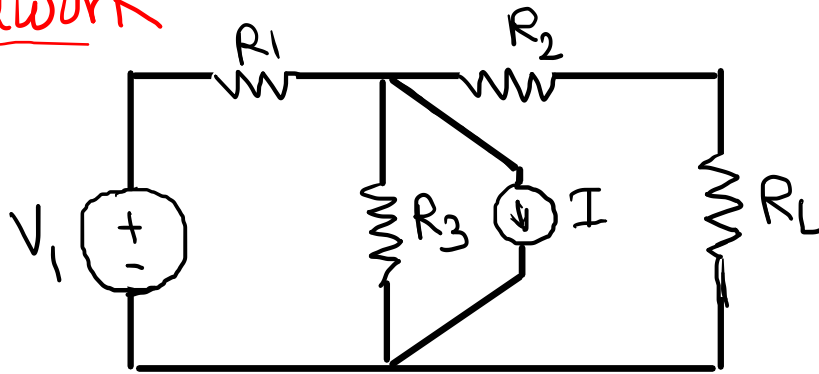


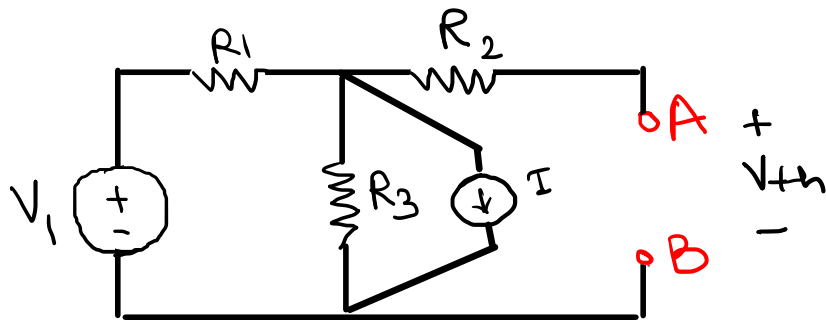1. Remove load resistance R_L from the given network




2. Find V_{th} i.e. the open circuit voltage between the terminals (A-B) from where the load is removed using any suitable method (mesh, nodal, source transformation etc..)

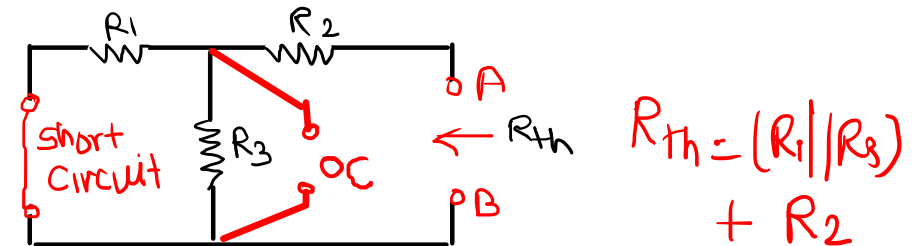
3. Find R_{th} i.e. resistance looking back into the network from the terminals (A-B) from where the load is removed and energy sources replaced by their internal resistances.



4. Draw thevenin's equivalent circuit

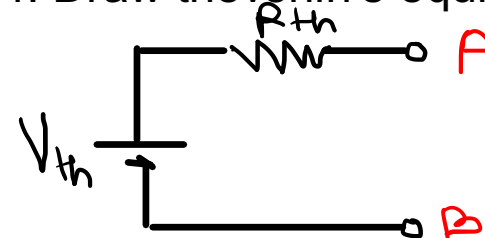

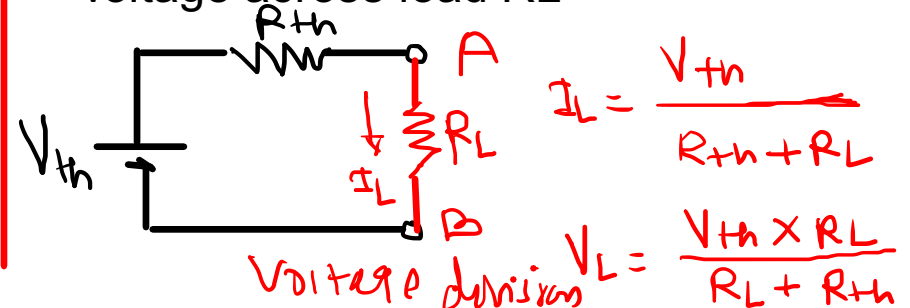
5. Connect the load R_L and find current/voltage across load R_L



Thevenin's Theorem

Q.1 Find current flowing through 10 Ohm resistance using Thevenin's Theorem

$$I_D = 0.464A$$

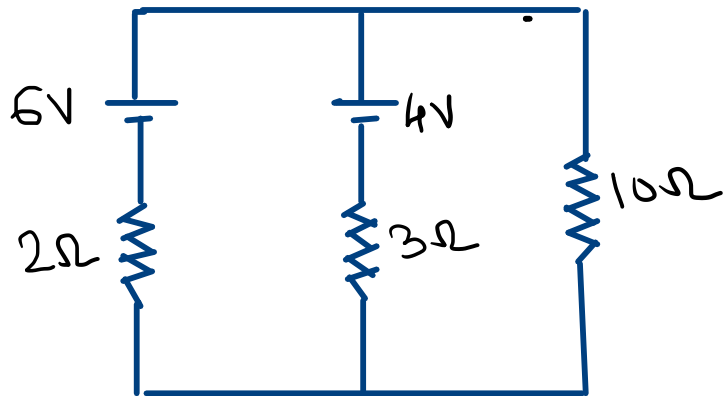

② Find V_{th} .

$$V_{th} - 4 - V_{3\Omega} = 0$$

$$V_{th} = 4 + V_{3\Omega}$$

KVL to loop to find I


$$-4 - 3I - 2I + 6 = 0$$

$$5I = 2 \quad \therefore I = \frac{2}{5} = 0.4A$$


$$V_{3\Omega} = 3 \times I = 3 \times 0.4 = 1.2V$$

$$V_{th} = 4 + 1.2 = 5.2V$$

① Remove load $R_L = 10\Omega$

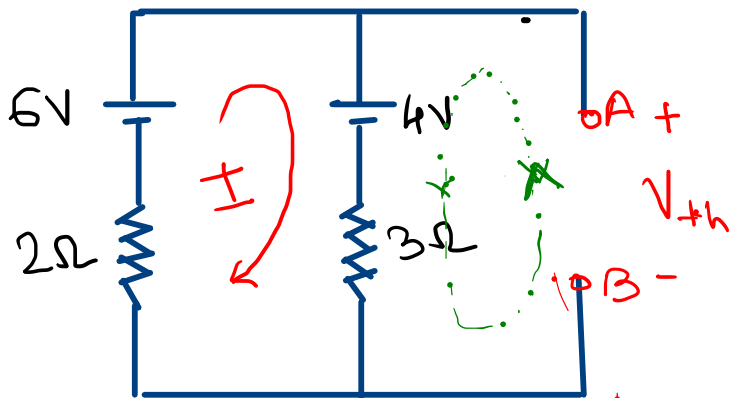

③ Find R_{th}

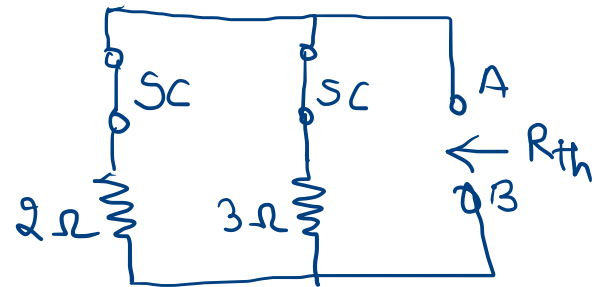

$$R_{th} = 3 \parallel 2$$


$$= \frac{3 \times 2}{3 + 2}$$

$$R_{th} = \frac{6}{5} = 1.2\Omega$$


Thevenin's Theorem

Q.1 Find current flowing through 10 Ohm resistance using Thevenin's Theorem


$$I_{10} = 0.464A$$

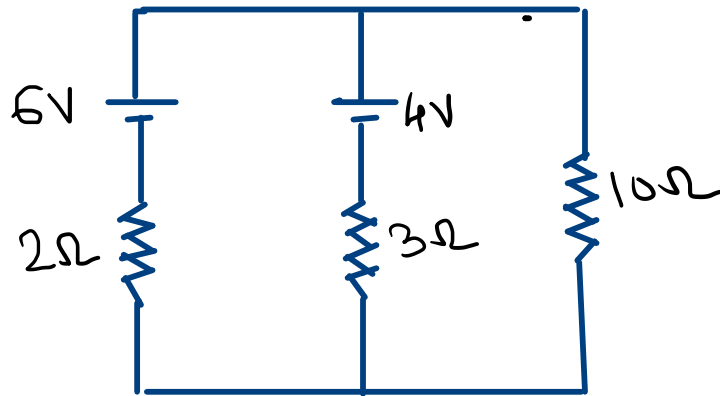


① Remove load $R_L = 10\Omega$

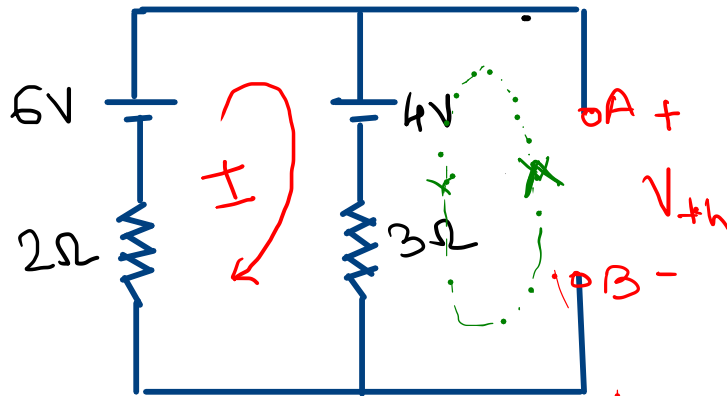

④ Draw Thevenin's Equivalent circuit

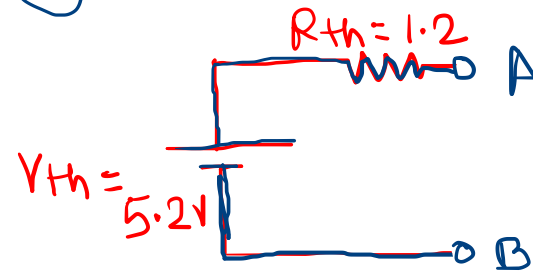

⑤ Connect the load & find current

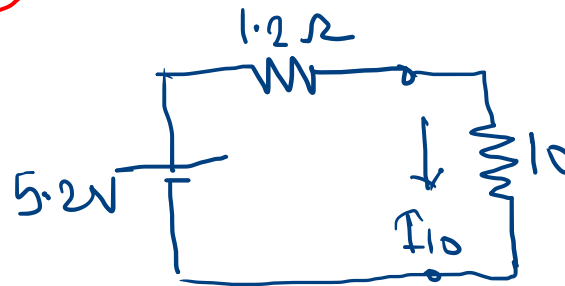

$$I_{10} = \frac{5.2}{1.2 + 10} = 0.464A$$


Thevenin's Theorem

Example:- 2. Find current through $R_L = 15 \text{ Ohm}$ resistor in the following network.


$$V_{th} = 10.9 \text{ V}$$

$$I_{L} = 0.4 \text{ A}$$

$$R_{th} = 8.33 \text{ } \Omega$$

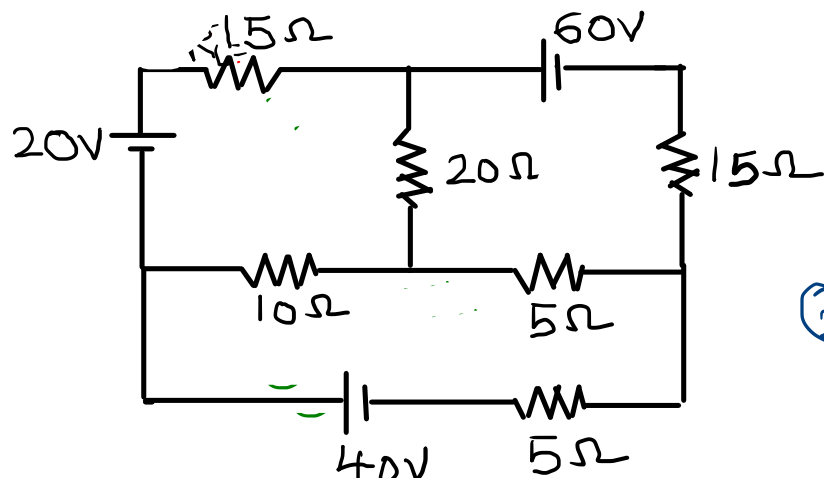

① Remove $R_L = 15 \Omega$

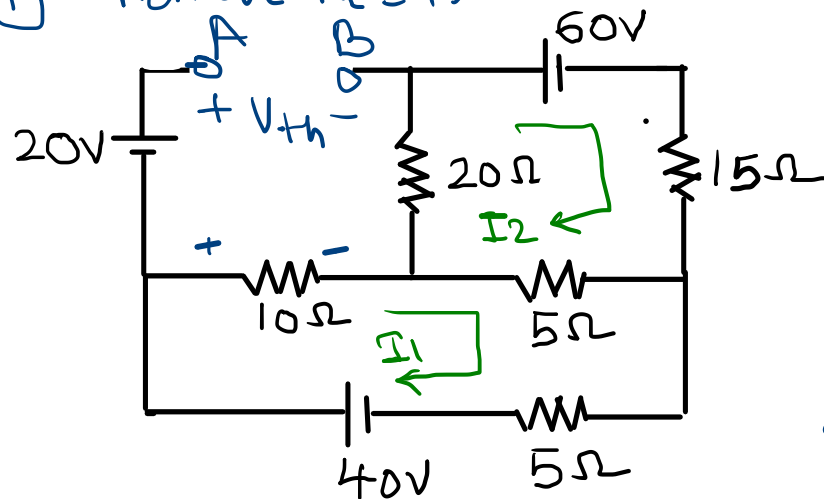

$$V_{th} = 20 - V_{10\Omega} - V_{20\Omega} = 0$$

$$V_{th} = 20 + V_{10\Omega} + V_{20\Omega}$$

② To find V_{th}

Solving using mesh Analysis

KVL to mesh ①

$$40 - 10I_1 - 5(I_1 - I_2) - 5I_1 = 0$$

$$20I_1 - 5I_2 = 40 \text{ --- (1)}$$

KVL to mesh ②

$$-60 - 15I_2 - 5(I_2 - I_1) - 20I_2 = 0$$

$$5I_1 - 40I_2 = 60 \text{ --- (2)}$$

Solving ① & ② $I_1 = 1.67 \text{ A}$ $I_2 = -1.29 \text{ A}$

Thevenin's Theorem

Example:- 2.


$$V_{th} = 20 + V_{10\Omega} + V_{20\Omega}$$

$$V_{10\Omega} = 1.67 \times 10 = 16.7V$$

$$V_{20} = -1.29 \times 20 = -25.8V$$

$$V_{th} = 20 + 16.7 - 25.8 = 10.9V$$

③ Find R_{th}

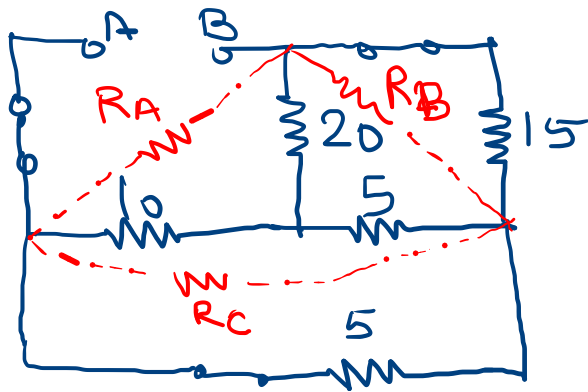

Star to Delta Transformation



$$\Sigma R = R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$R_A = \frac{\Sigma R}{R_2}$$

$$R_B = \frac{\Sigma R}{R_3}$$

$$R_C = \frac{\Sigma R}{R_1}$$

$$\Sigma R = 10 \times 20 + 20 \times 5 + 10 \times 5$$

$$\Sigma R = 200 + 100 + 50 = 350\Omega$$

$$R_A = \frac{350}{5} = 70\Omega$$

$$R_B = \frac{350}{10} = 35\Omega$$

$$R_C = \frac{350}{20} = 17.5\Omega$$

$$V_{th} = 10.9V$$

$$I_{sc} = 0.40A$$

$$R_{th} = 8.33\Omega$$

Thevenin's Theorem




Example:- 2.

$$V_{th} = 10.9V$$

$$I_{15} = 0.4A$$

$$R_{th} = 8.33\Omega$$


③ Find R_{th}

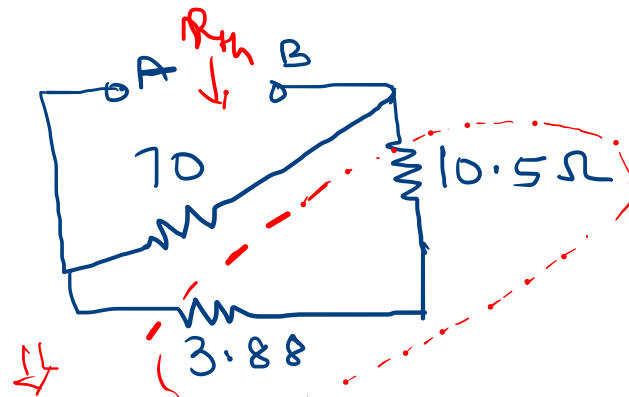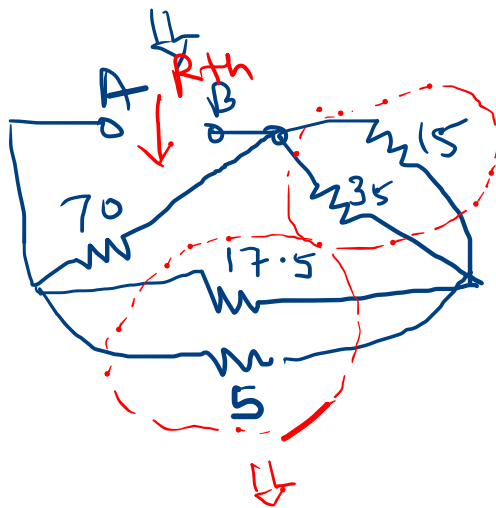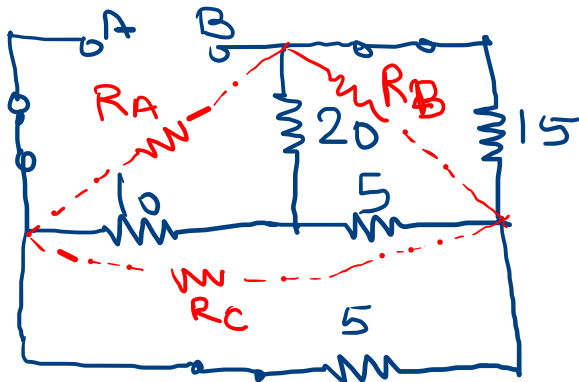

$$R_{th} = 70 \parallel 14.38$$

$$R_{th} = 11.9\Omega$$

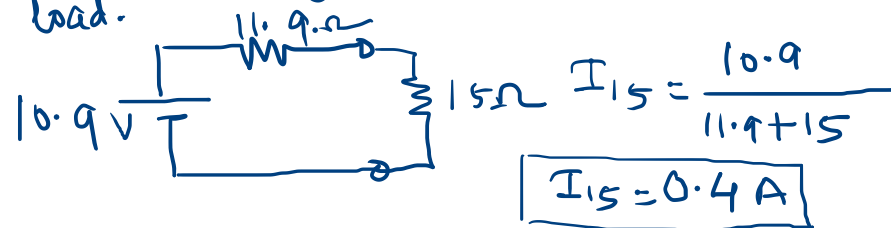④ Draw Thevenin's equivalent circuit & Connect load.




$$I_{15} = \frac{10.9}{11.9 + 15}$$


$$I_{15} = 0.4A$$

Thevenin's Theorem

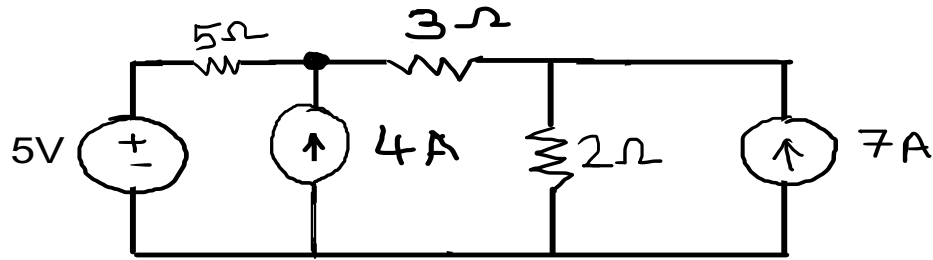Example:- 3. Find voltage across 2 Ohm resistor in the flowing network.



⇒ ① Remove the load $R_L = 2\Omega$

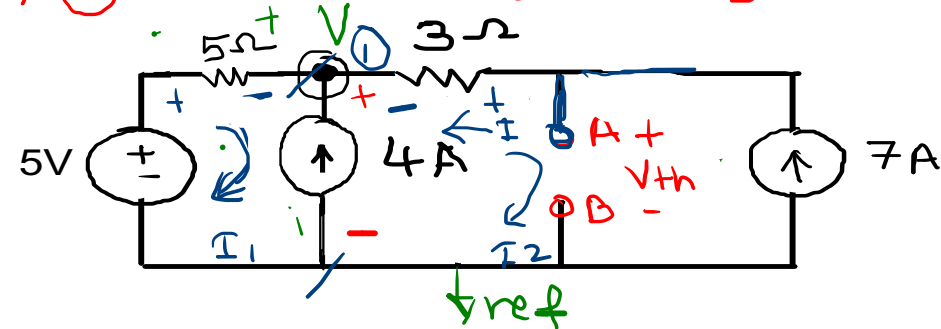

⇒ ② Find V_{th}

$$\underline{V_{th}} - 3I - V_{4A} = 0$$

Using Nodal Analysis
KCL at node ①

$$\underline{7+4} = \frac{V-5}{5}$$

$$11 = \frac{V-5}{5} \text{ OR } V-5 = 55$$

$$V = 60V. \quad V_{4A} = V = 60V$$

$$I = 7A$$

$$V_{th} = 3 \times I + V_{4A}$$

$$V_{th} = 3 \times 7 + 60 = 81V$$

using mesh Analysis.

$$I_2 = -7A$$

$$I_1 + 4 = I_2 \text{ OR } I_1 = -7 - 4 = \underline{\underline{-11A}}$$

$$V_{4A} = 11 \times 5 + 5 = 60$$

$$V_{th} = 3 \times 7 + 60 = 81V$$

$$V_{th} = 81V$$


$$R_{th} = 8\Omega$$

$$V_{2\Omega} = 16.2V$$

Thevenin's Theorem


Example:- 3.

③ Find R_{th}

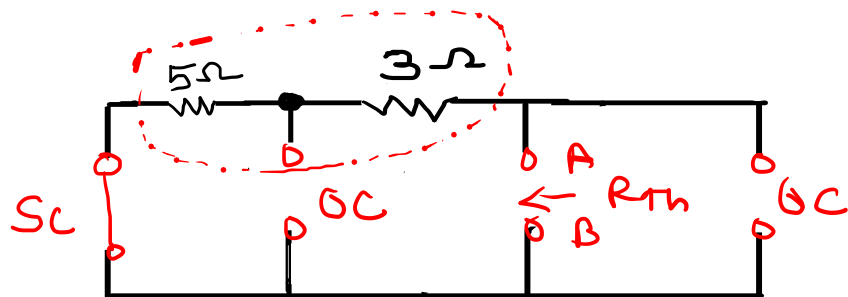

$$R_{th} = 5 + 3 = 8\Omega$$

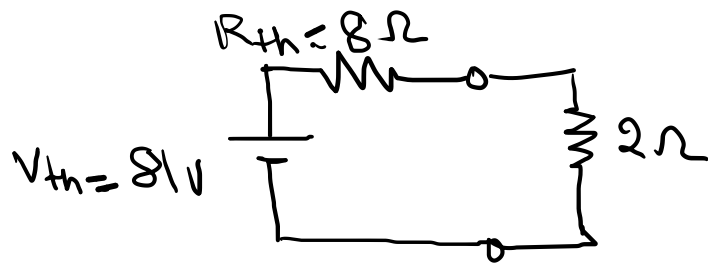④ Draw Thevenin's Equivalent Circuit & Connect load.



using voltage division formula

$$V_{2\Omega} = \frac{2 \times 81}{2 + 8}$$

$$V_{2\Omega} = \frac{2 \times 81}{10}$$

$$V_{2\Omega} = 16.2V$$

$$V_{th} = 81V$$

$$R_{th} = 8\Omega$$

$$V_{2\Omega} = 16.2V$$